

***Design, Simulation, and Bandwidth Extension  
Methods for Fractional-N Frequency Synthesizers***

***ISSCC 2005 GIRAFE Forum on  
Clock and Frequency Generation***

**Michael Perrott  
Massachusetts Institute of Technology  
February 6, 2005**


**Copyright © 2005 by Michael H. Perrott  
All rights reserved.**

# *Outline*

---

- **Fundamentals**
- **Proposed Bandwidth Extension Technique**
- **Design at the Transfer Function Level**
- **Simulation at the Behavioral Level**
- **Measured Results**

# What Is A Phase-Locked Loop?

 


de Bellescize  
Onde Electr, Vol. 11  
1932

- VCO → produces variable frequency output
- Reference → provides input frequency/phase
- PFD → compares phase of ref and VCO output
- Charge pump → simplifies loop filter implementation
- Loop filter → smooths PFD signal


**Objective: “Lock” VCO phase to reference phase**

# Method of Phase Detection

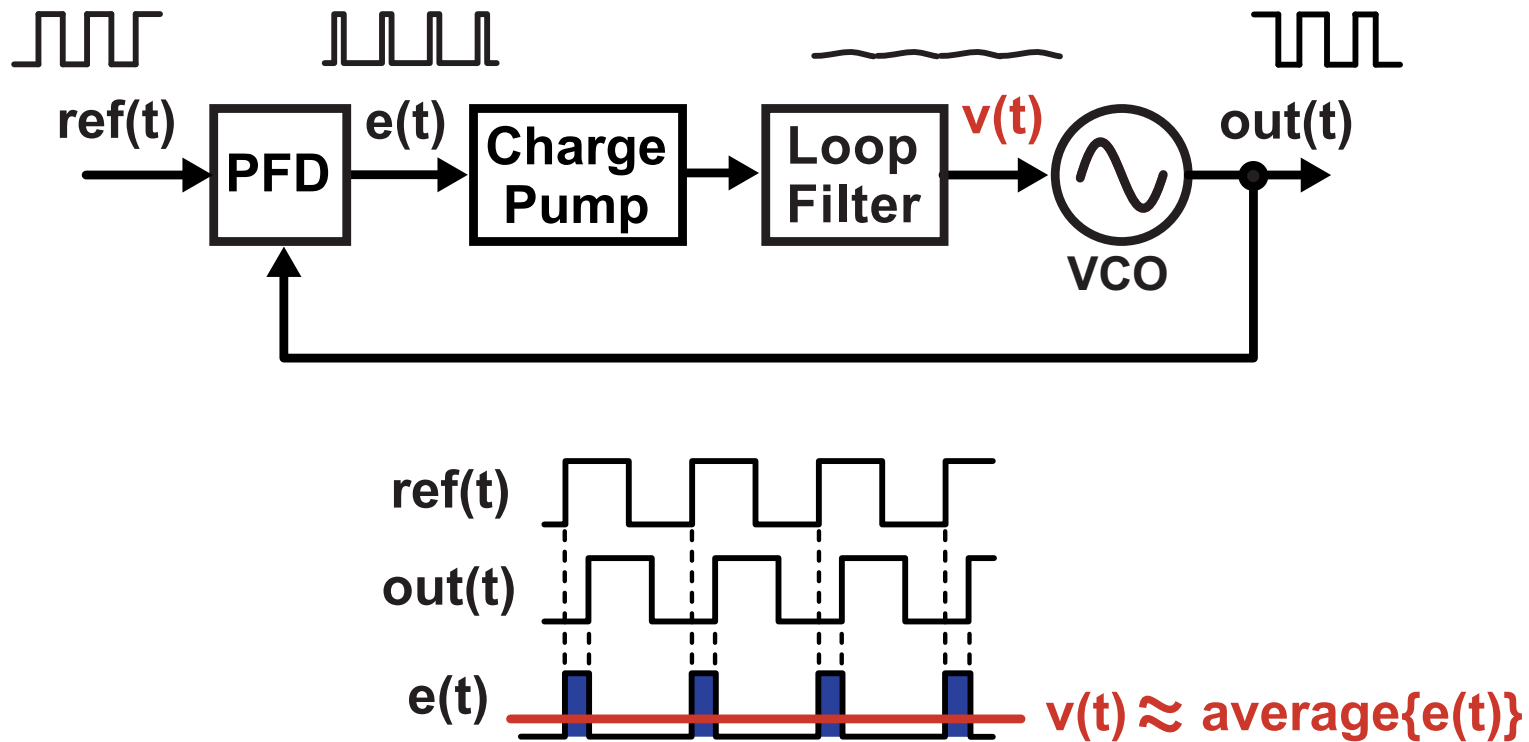


- PFD output consists of pulses whose width is proportional to the phase error
  - Phase is only observable at edges
- Smooth PFD output to produce input voltage to VCO

# Impact of Changes in Phase Error

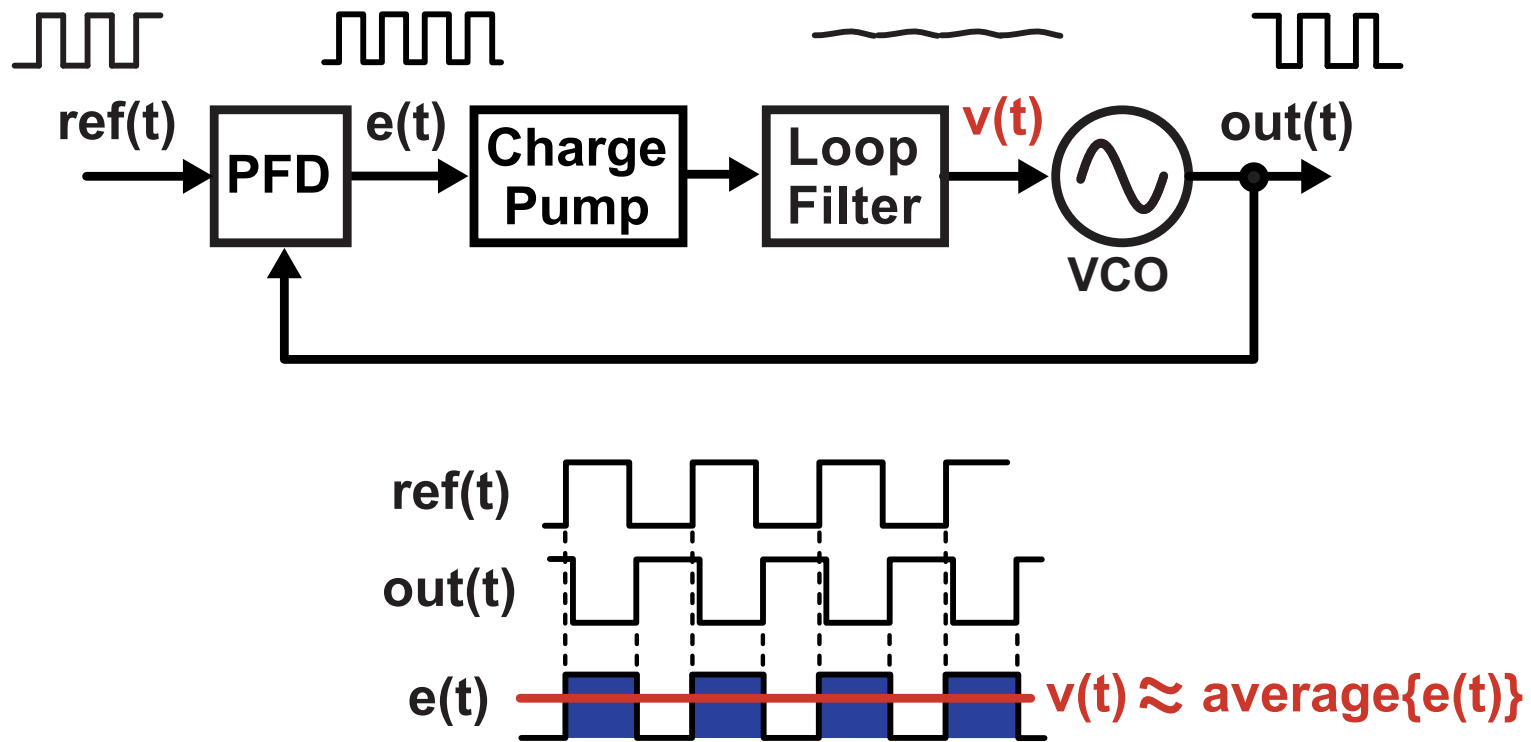


- Pulse width varies according to phase difference
- VCO input voltage changes accordingly
  - Adjusts VCO frequency and phase

# Phase Lock Implies Frequency Lock

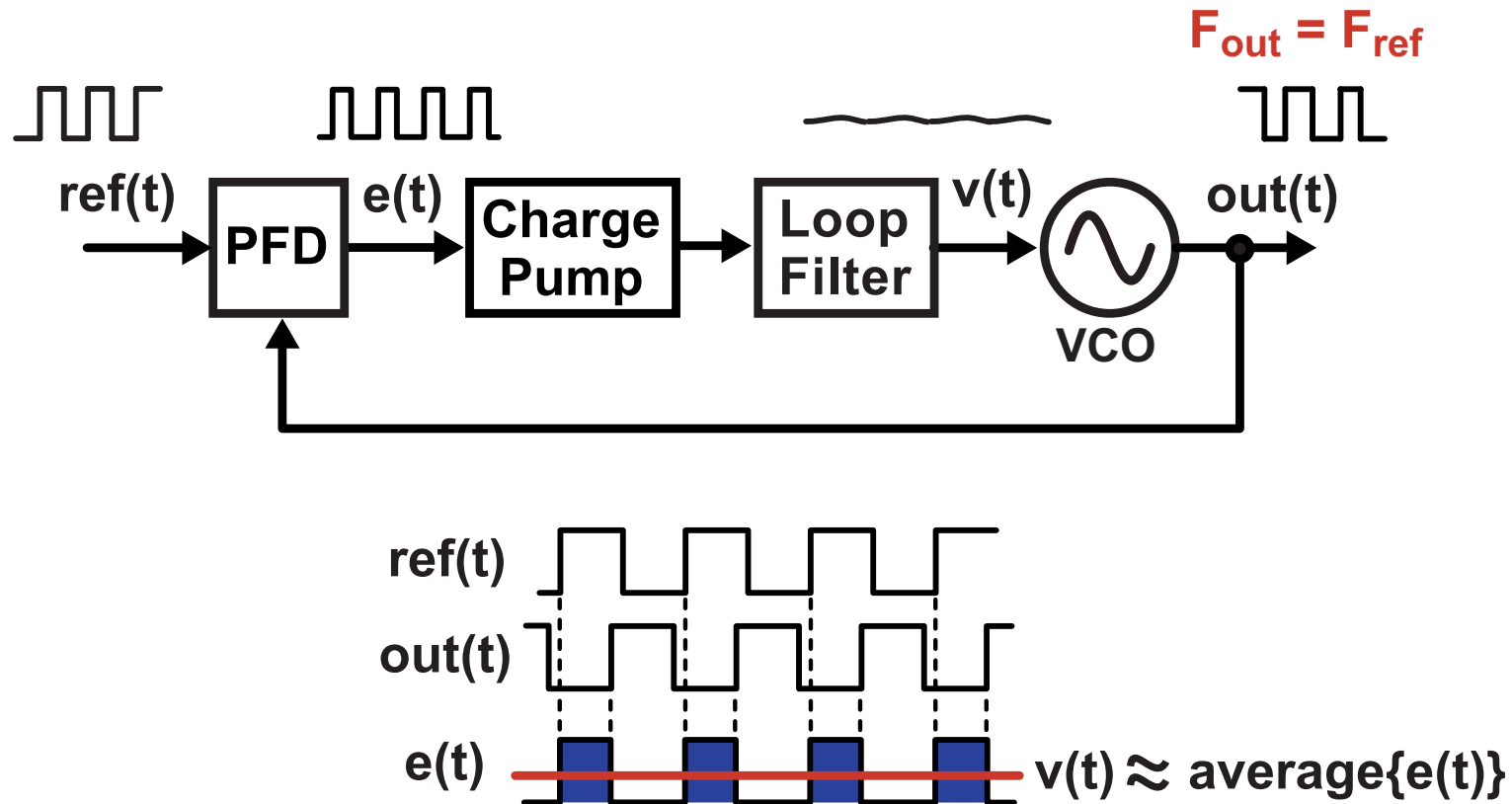


- Any error in frequency leads to a steady accumulation of phase error

# Integer-N Frequency Synthesizer

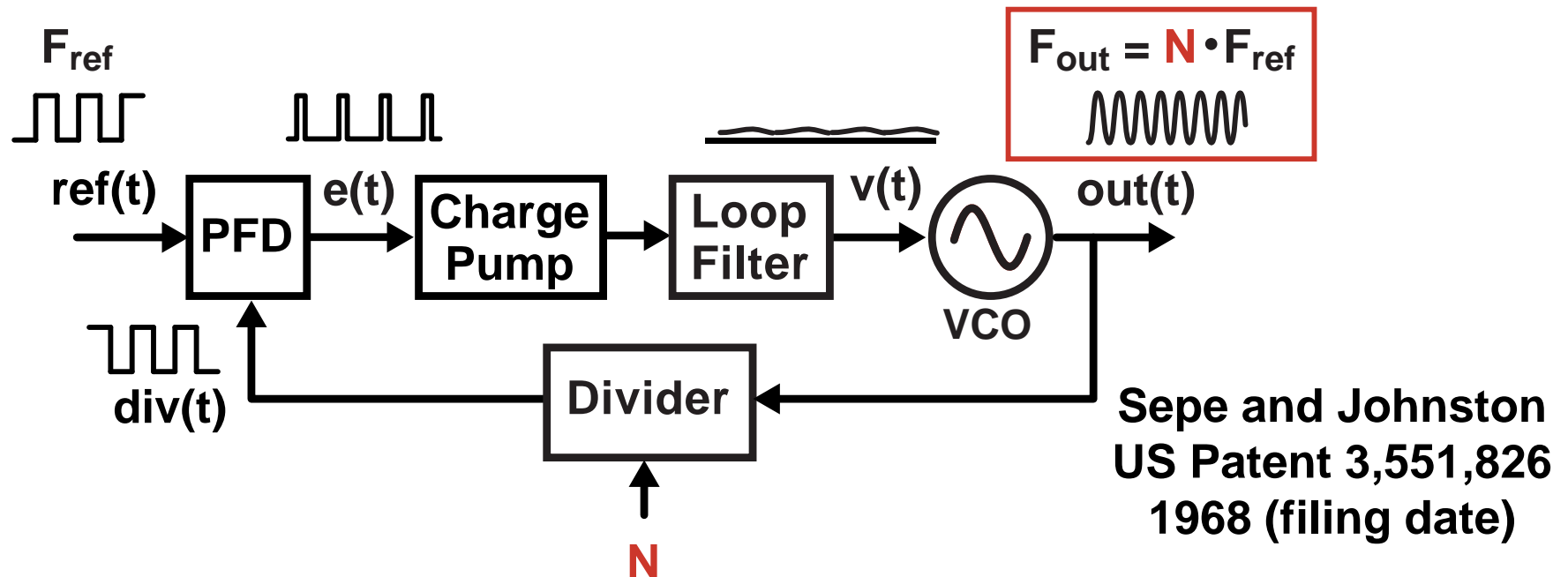

- Leverages frequency divider to create “indirect” frequency multiplication
  - Allows digital adjustment of output frequency in increments of the reference frequency


## Issue

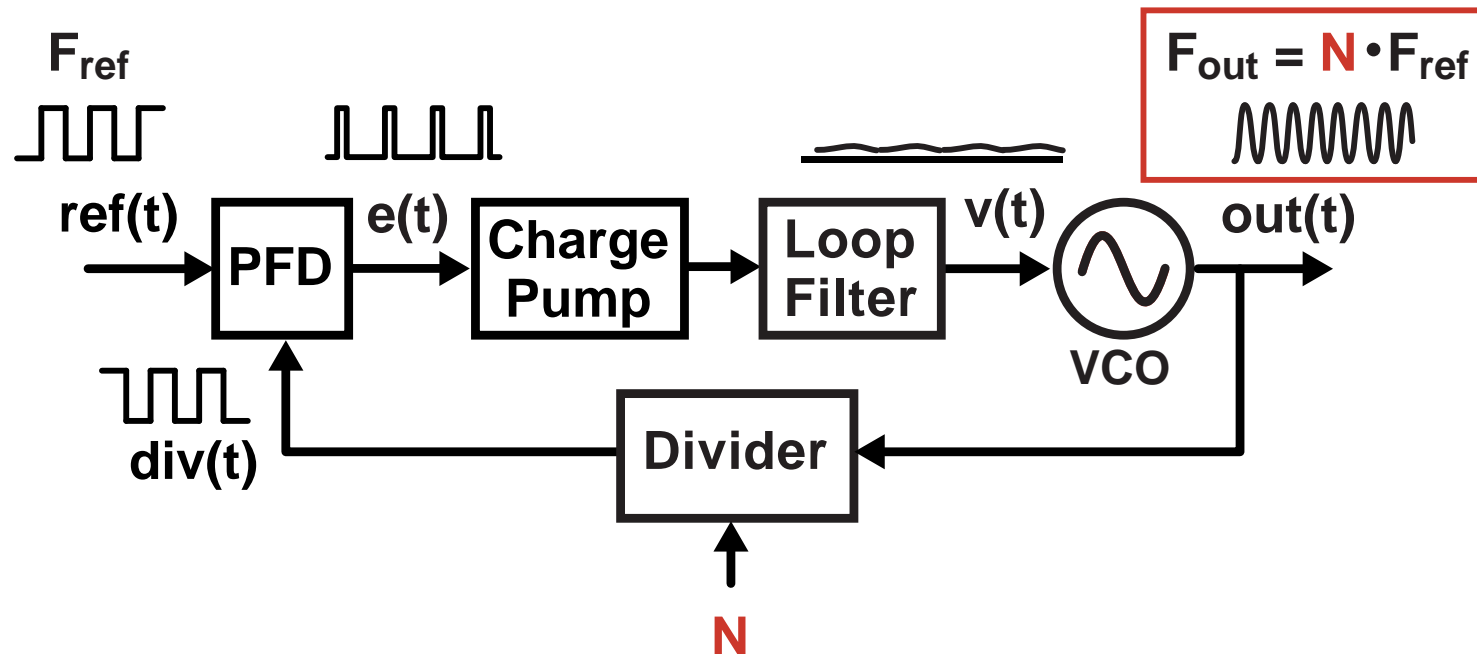

- **Key constraint: Divider value,  $N$ , must be integer**
  - High frequency resolution requires low  $F_{ref}$
  - High PLL bandwidth requires high  $F_{ref}$

**Tradeoff: Frequency resolution vs PLL bandwidth**


# Fractional-N Frequency Synthesis

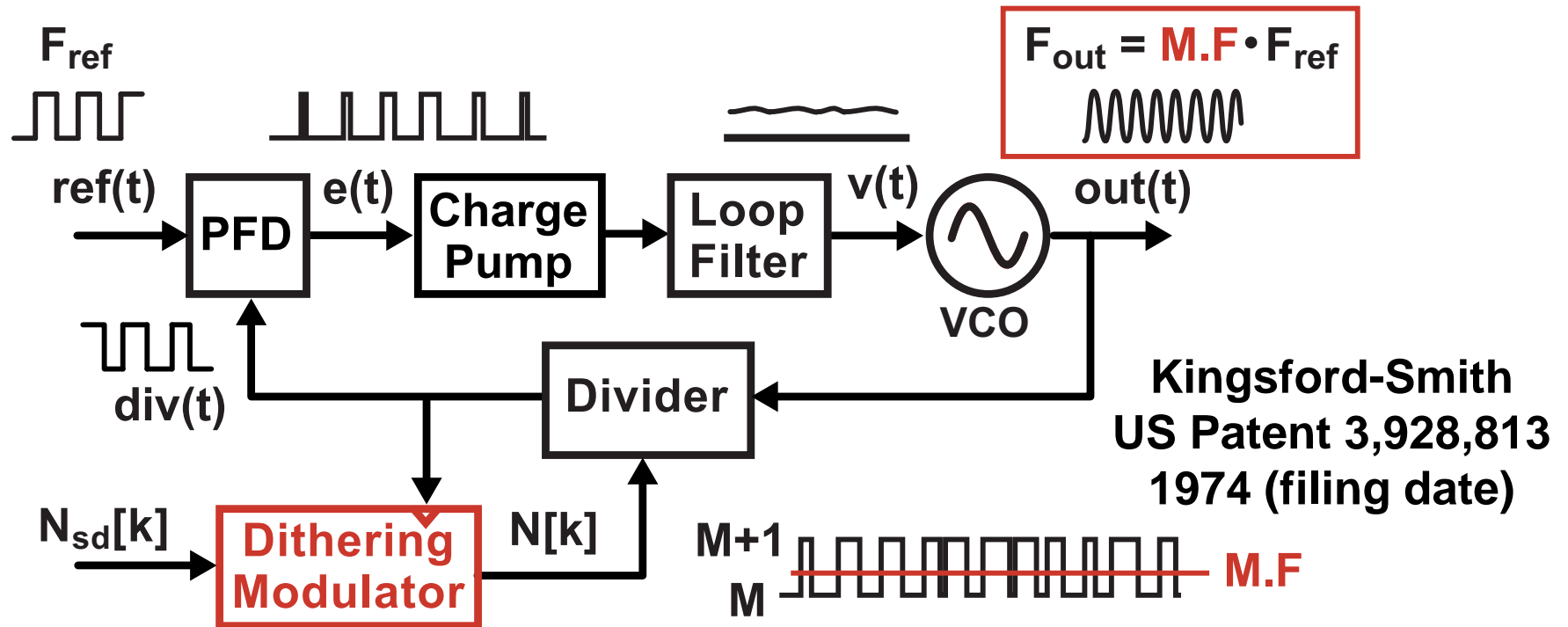

- Divide value is dithered between integer values
- Fractional divide values can be realized!


Very high frequency resolution
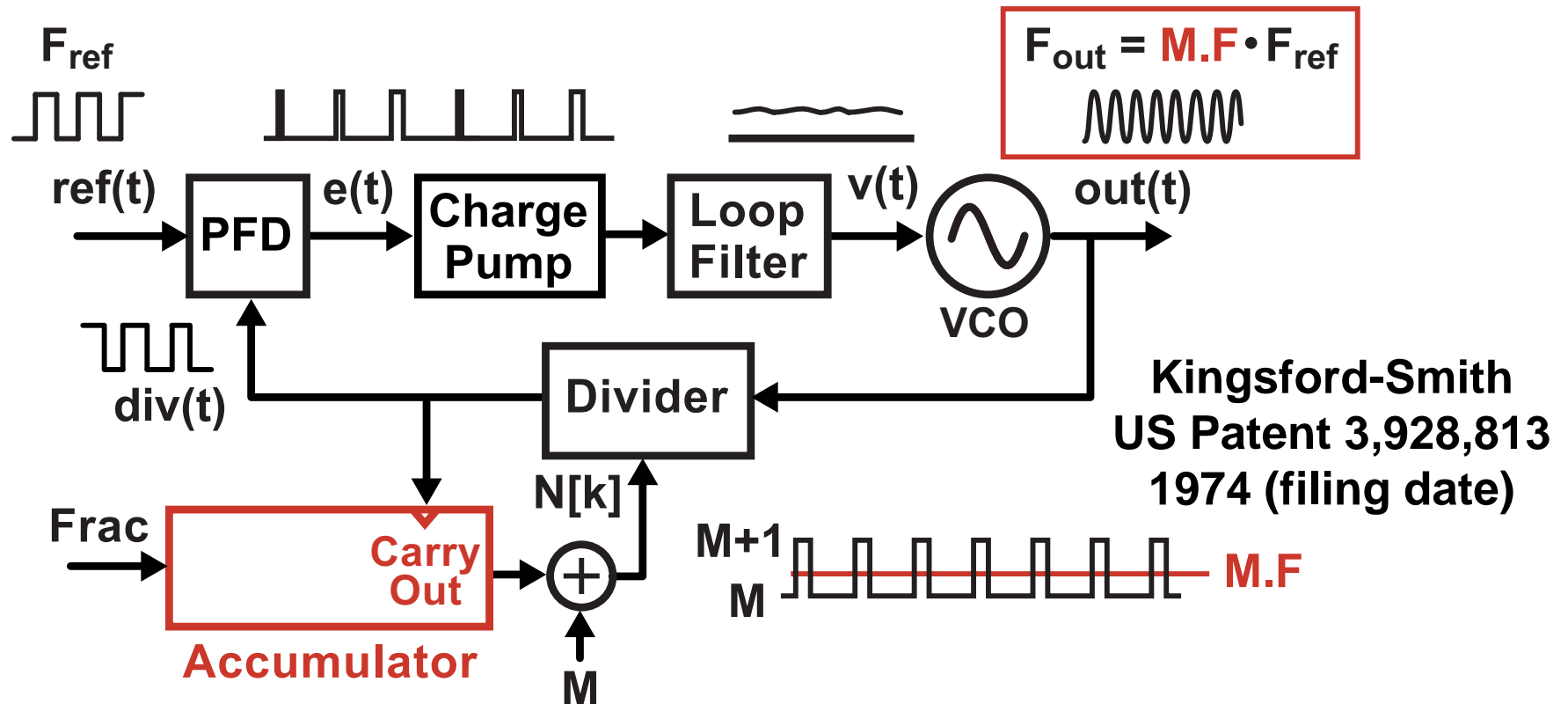
# Classical Fractional-N Synthesizer Architecture




- Use an accumulator to perform dithering operation
  - Fractional input value fed into accumulator
  - Carry out bit of accumulator fed into divider
 
## Integer-N Synthesizer Signals with $F_{out} = 4.25F_{ref}$




- **Constant divide value of  $N = 4$  leads to frequency error**
  - **Error pulse widths increase as phase error accumulates**
 
## Fractional-N Synthesizer Signals with $F_{out} = 4.25F_{ref}$




- **Dithering allows average divide value of  $N = 4.25$** 
  - **Reset phase error by periodically “swallowing” a VCO cycle**
    - Achieved by dividing by 5 every 4 reference cycles
 
# Key Observations for Classical Fractional-N Dithering




- The instantaneous phase error always remains less than one VCO cycle
- We can directly relate the phase error to the residue of the accumulator that is providing the dithering

# Accumulator Operation

 

- Carry out bit is asserted when accumulator residue reaches or surpasses its full scale value
- Accumulator residue corresponds to instantaneous phase error
  - ▬ Increments by the fractional value input into the accumulator


# The Issue of Spurious Tones

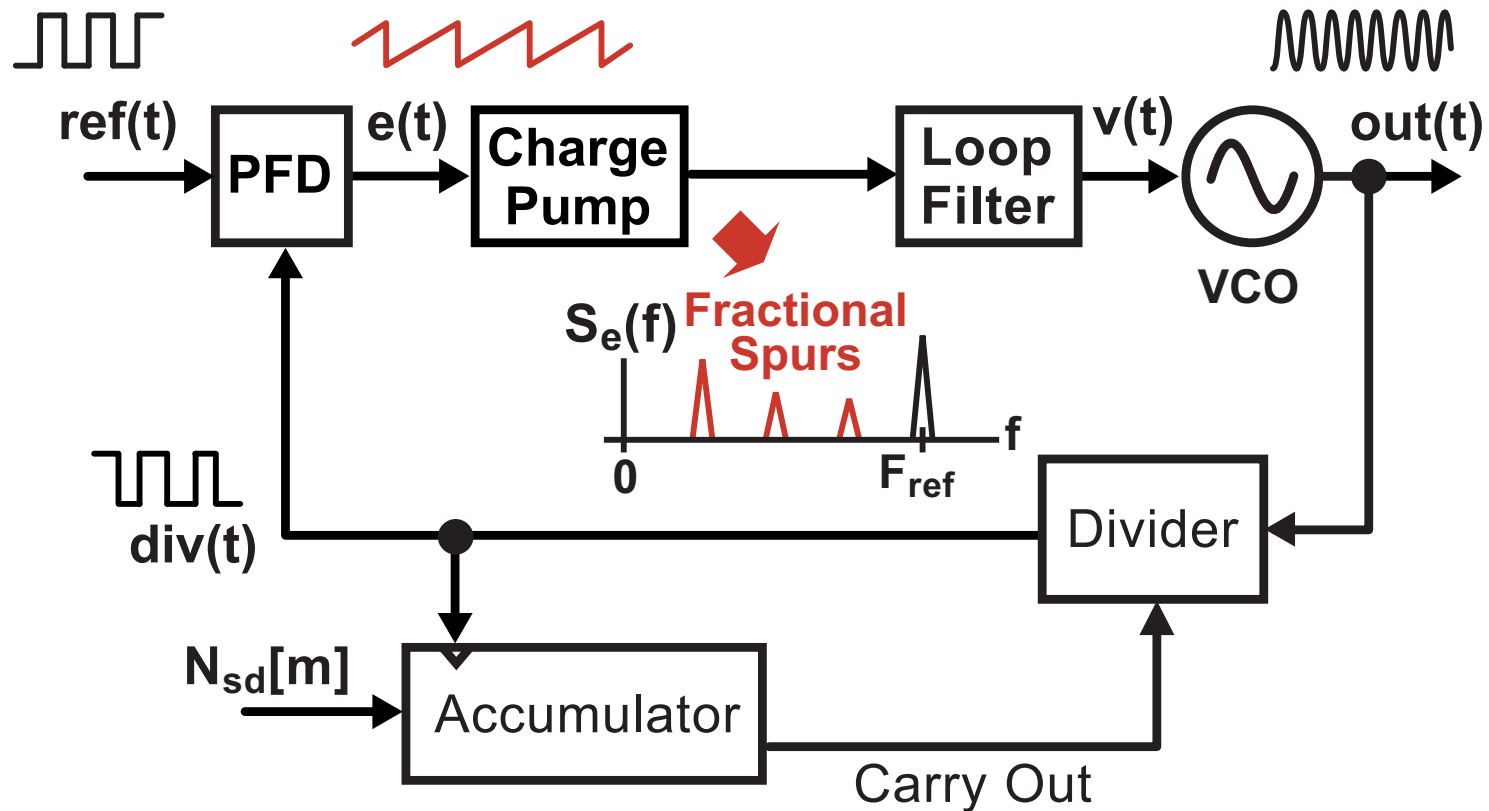

- PFD error waveform is periodic
  - Creates spurious tones in synthesizer output at lower frequencies than the reference
  - Ruins noise performance of the synthesizer




## The Problem With Phase Interpolation

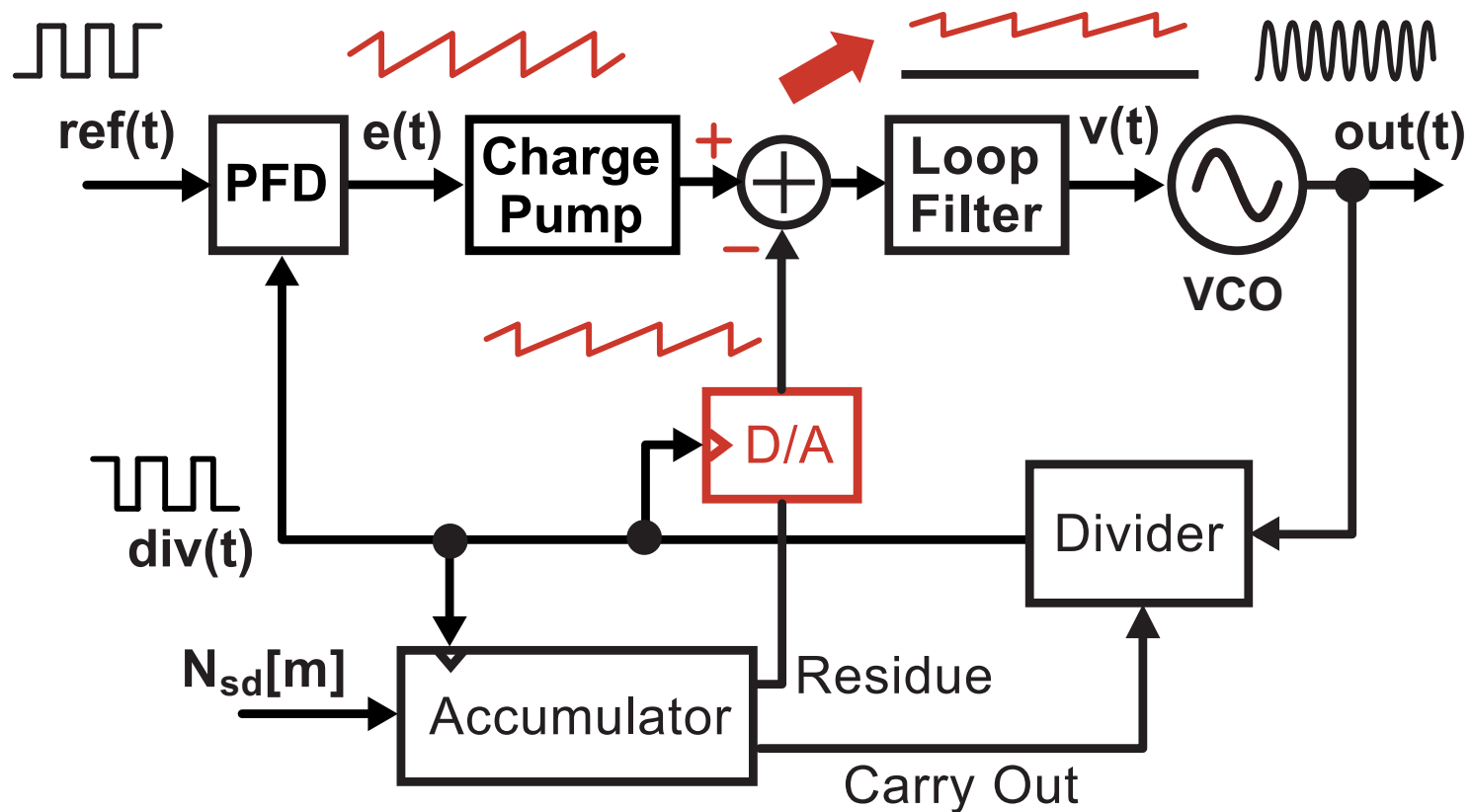

- Gain matching between PFD error and scaled D/A output must be extremely precise
  - Any mismatch will lead to spurious tones at PLL output

Matching issue prevented this technique from catching on

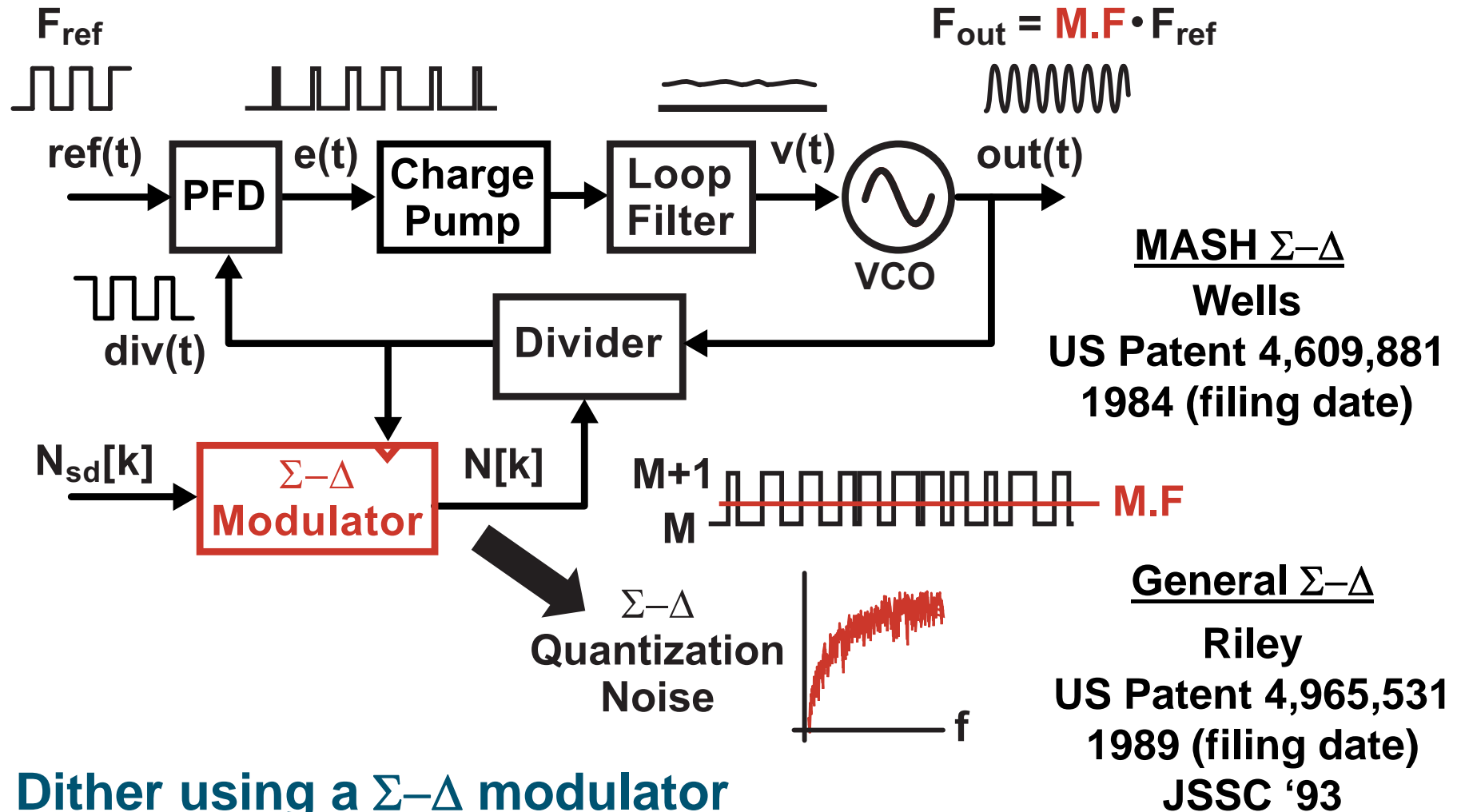
# $\Sigma\text{-}\Delta$ Fractional-N Frequency Synthesis



- **Dither using a  $\Sigma\text{-}\Delta$  modulator**


- Quantization noise is shaped to high frequencies
- Spur content of the quantization noise can be reduced to negligible levels
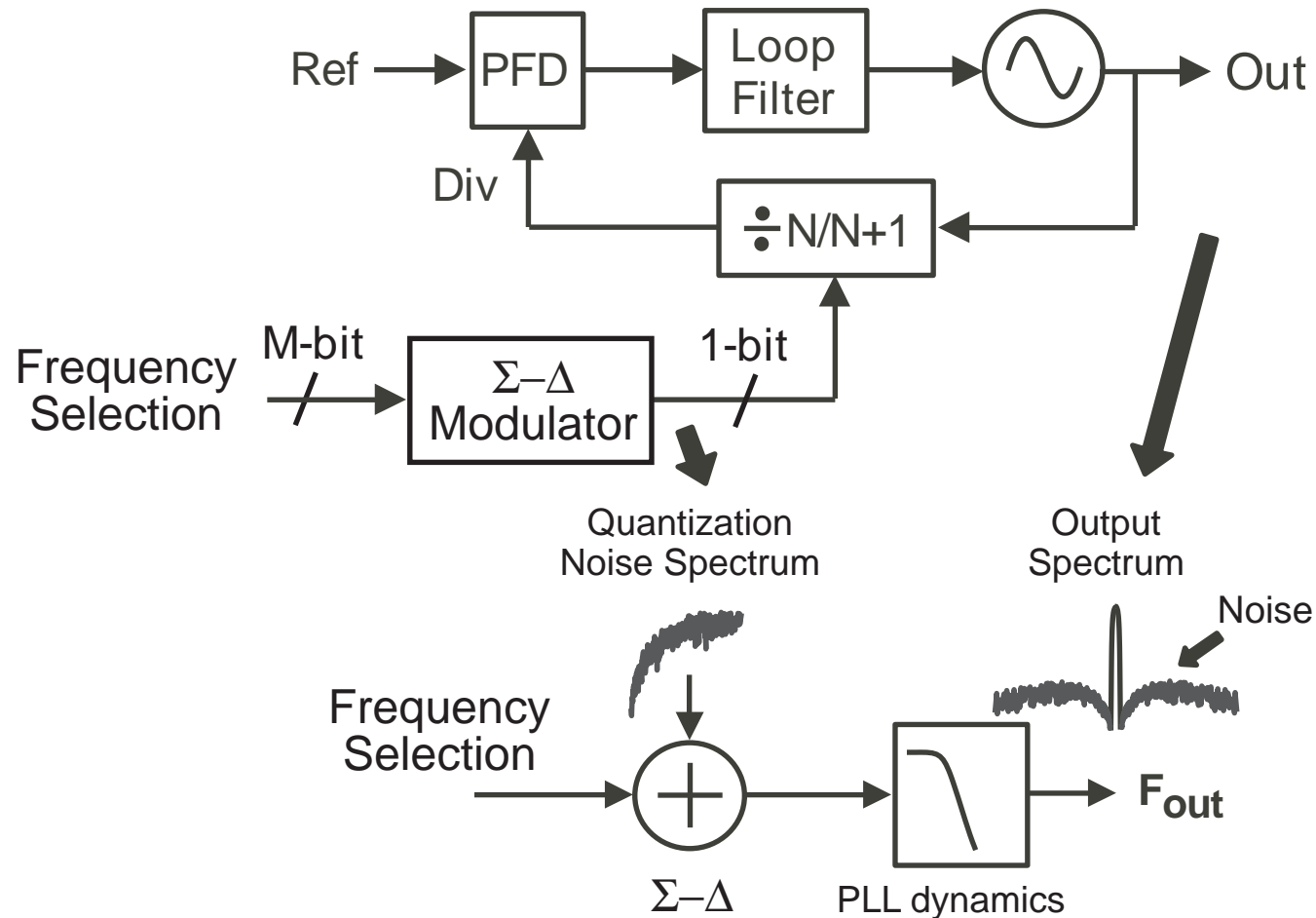
# Impact of $\Sigma\text{-}\Delta$ Quantization Noise on Synth. Output



- **Lowpass action of PLL dynamics suppresses the shaped  $\Sigma\text{-}\Delta$  quantization noise**

# Impact of Increasing the PLL Bandwidth

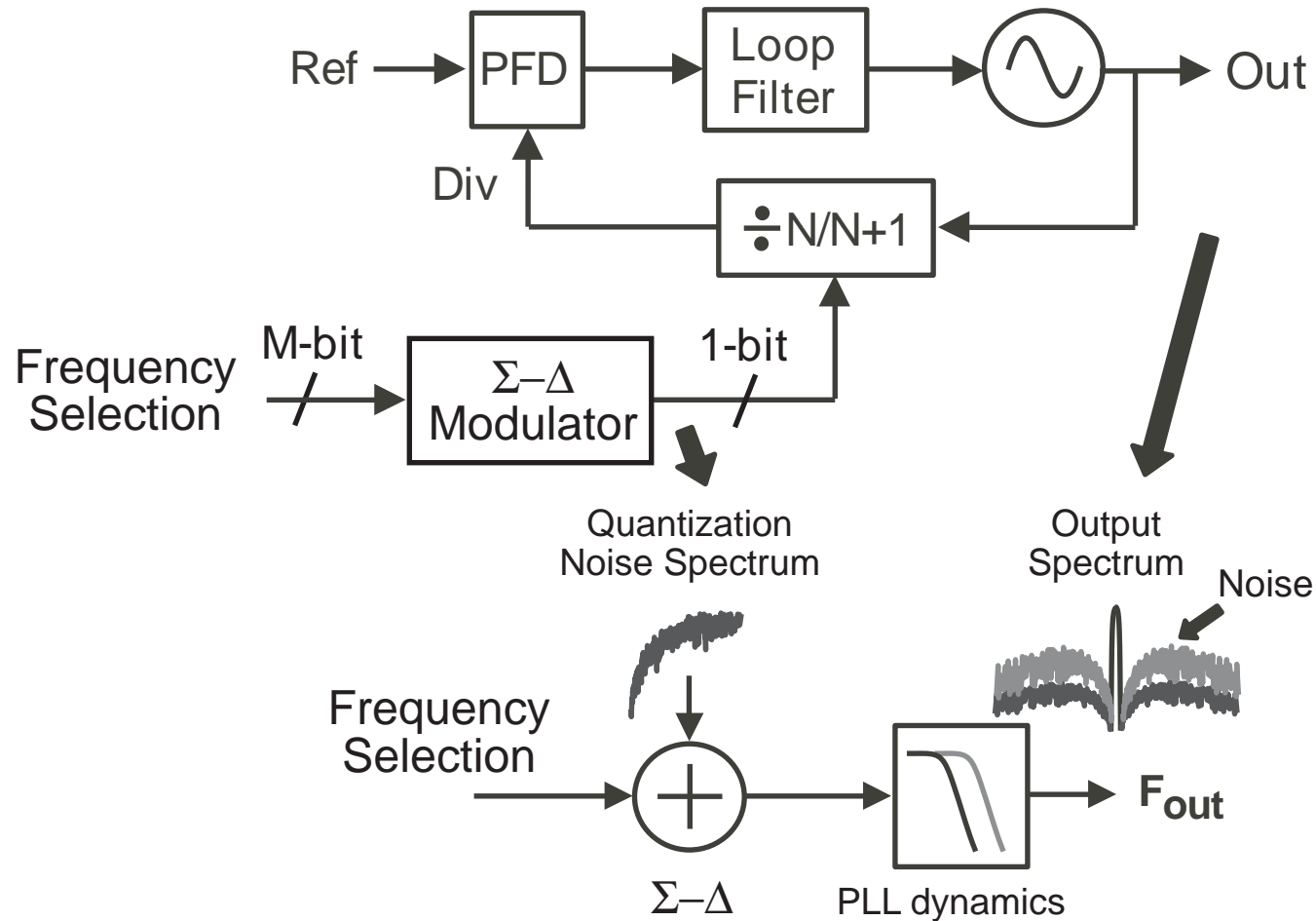

- Higher PLL bandwidth leads to less quantization noise suppression

**Tradeoff: Noise performance vs PLL bandwidth**

***Can We Do Better?***


## *Recent Approaches to Bandwidth Extension*

---

- [1] C. Park, O. Kim, and B. Kim, “A 1.8GHz Self-Calibrated Phase-Locked Loop with Precise I/Q Matching,” IEEE JSSC, May 2001.
- [2] K. Lee, et. al., “A Single Chip 2.4GHz Direct-Conversion CMOS Receiver for Wireless Local Loop Using Multiphase Reduced Frequency Conversion Technique ,” IEEE JSSC, May 2001.
- [3] S. Pamarti, L. Jansson, and I. Galton, “A Wideband 2.4GHz Delta-Sigma Fractional-N PLL With 1Mb/s In-Loop Modulation”, IEEE JSSC, Jan 2004
- [4] E. Temporiti, et. al., “A 700kHz Bandwidth  $\Sigma-\Delta$  Fractional-N Frequency Synthesizer with Spurs Compensation and Linearization Techniques for WCDMA Applications”, IEEE JSSC, Sept 2004


**We will focus on our own approach in this talk**

# Examine Classical Fractional-N Signals

 




- **Goal: eliminate the fractional spurs**

# Method 1: Vertical Compensation

 


- “Fill in” pulses so that they are constant area
  - Fractional spurs are eliminated!

## Method 2: Horizontal Compensation

   


 - Use constant width pulses of varying height to achieve constant area pulses
  - Largely eliminates fractional spurs



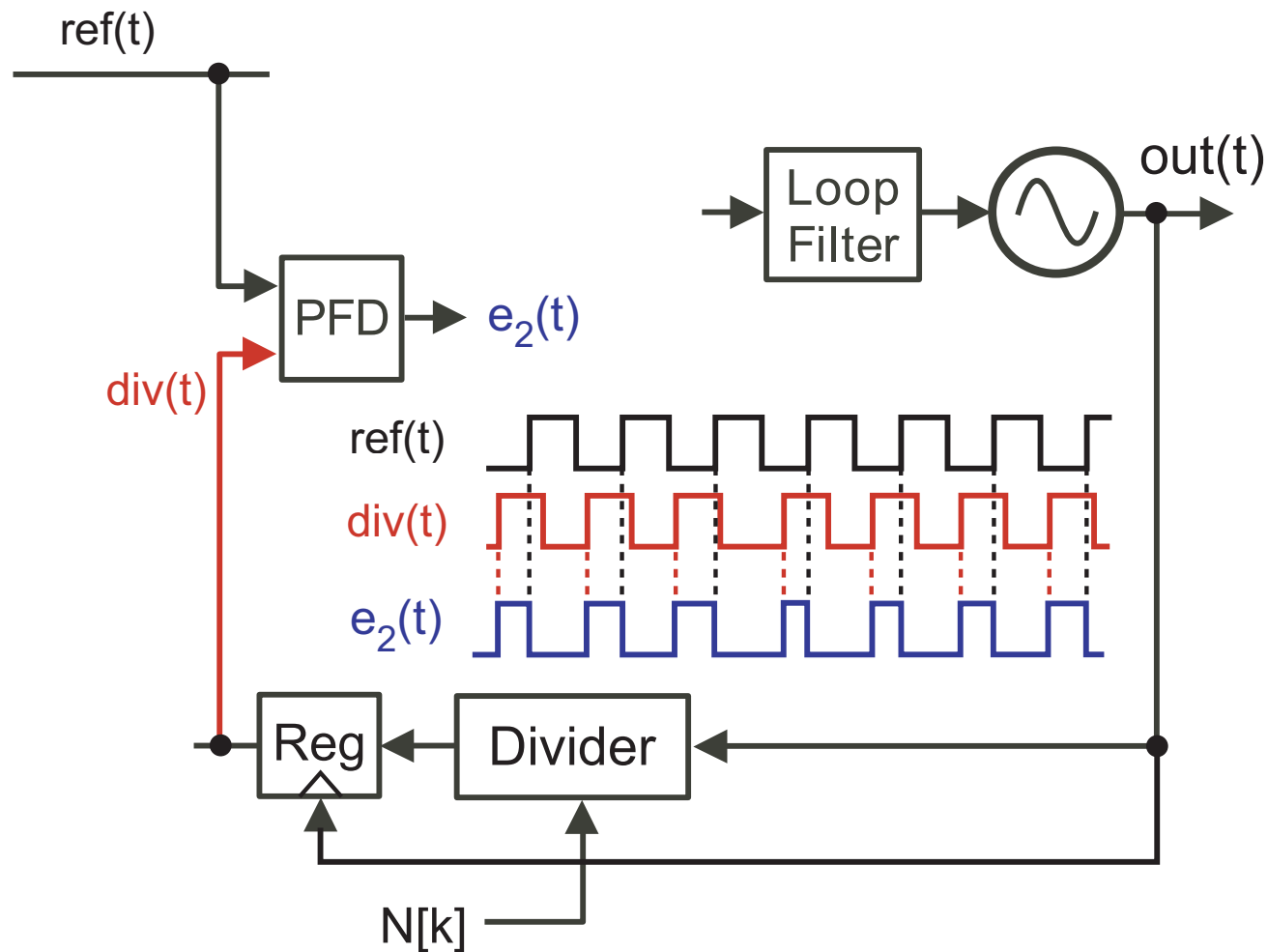
# Implementation of Horizontal Cancellation


- We begin with the basic fractional-N structure



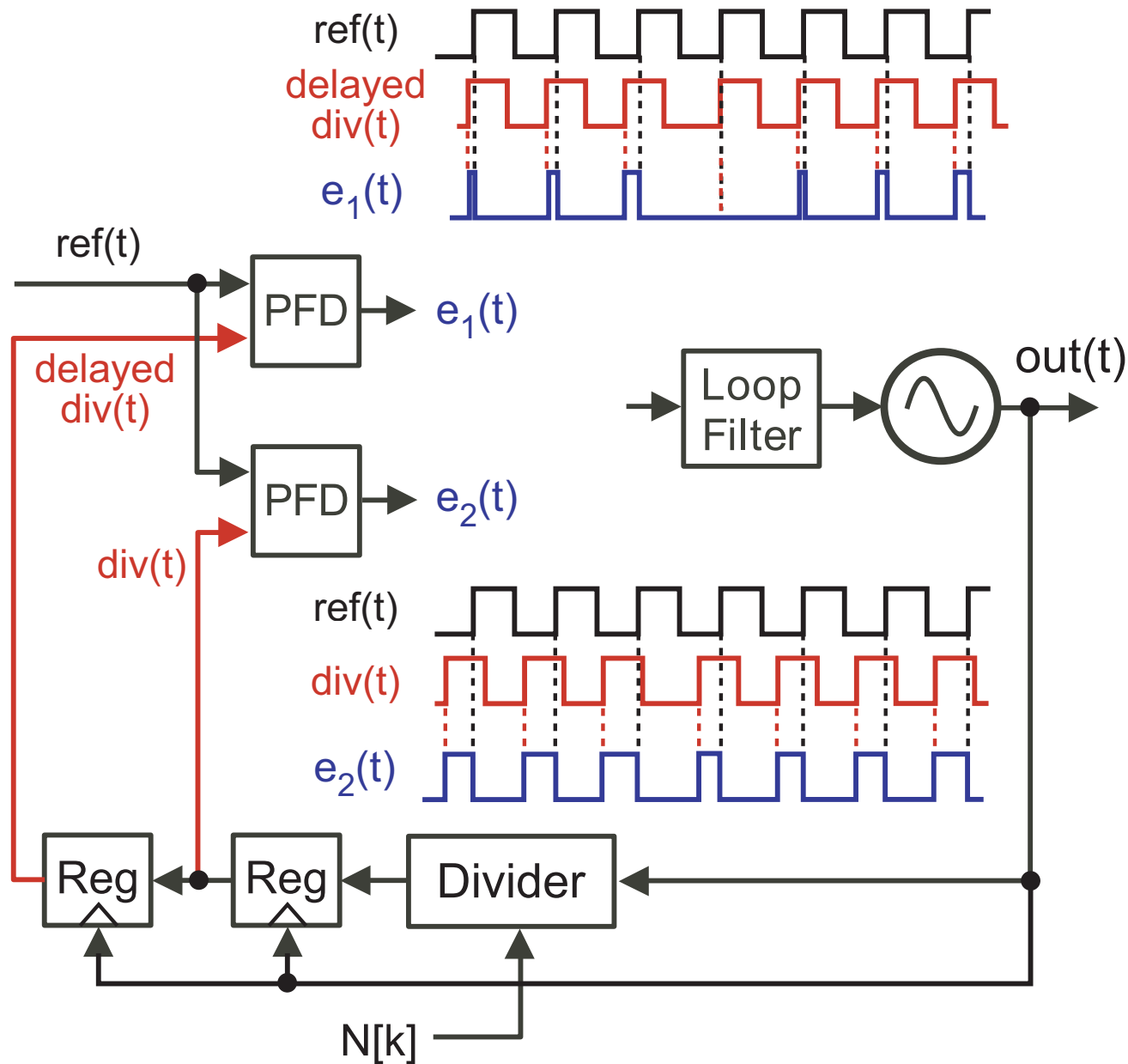
# Add a Second PFD with Delayed Divider Signal


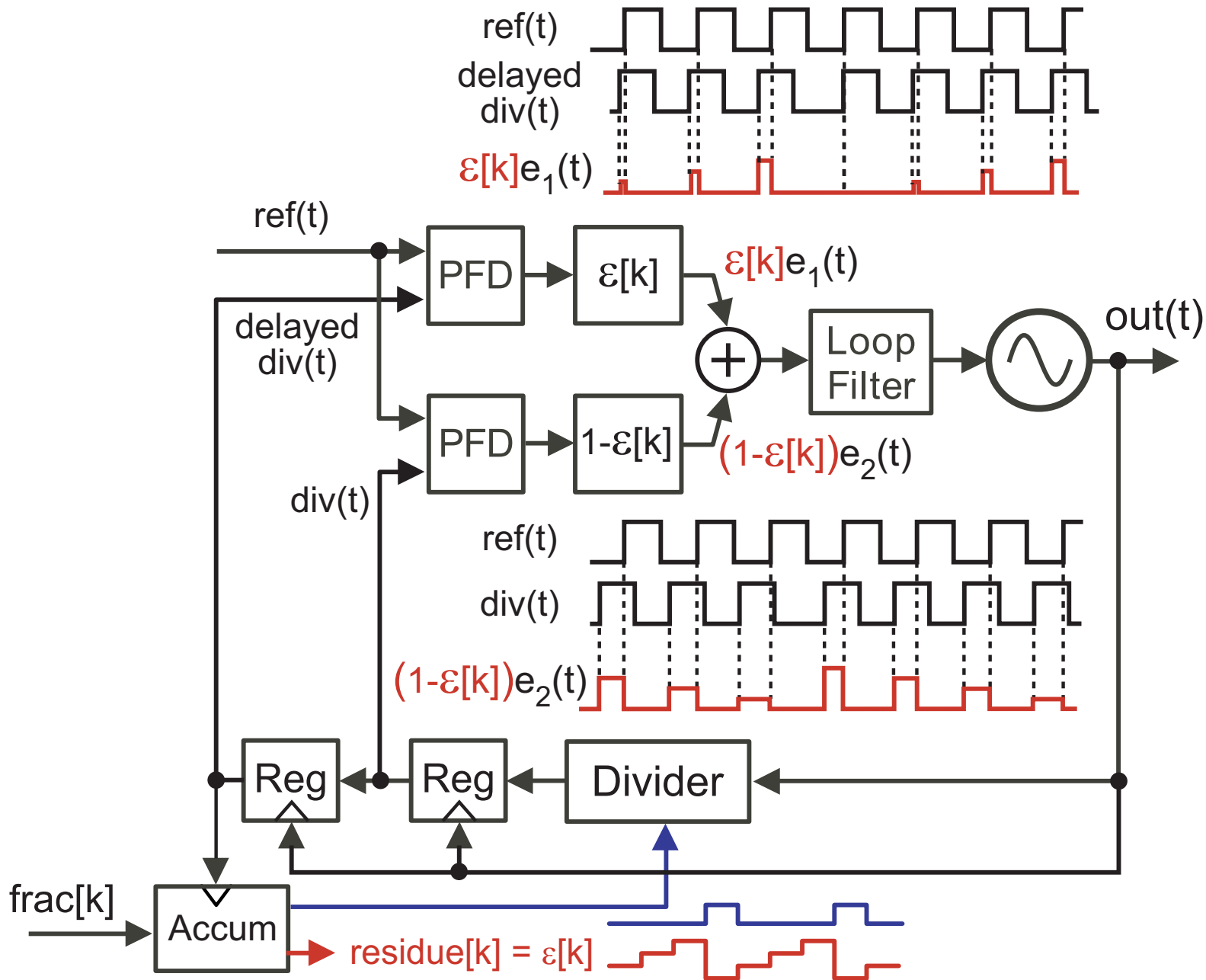
# Scale Error Pulses According to Accumulator Residue



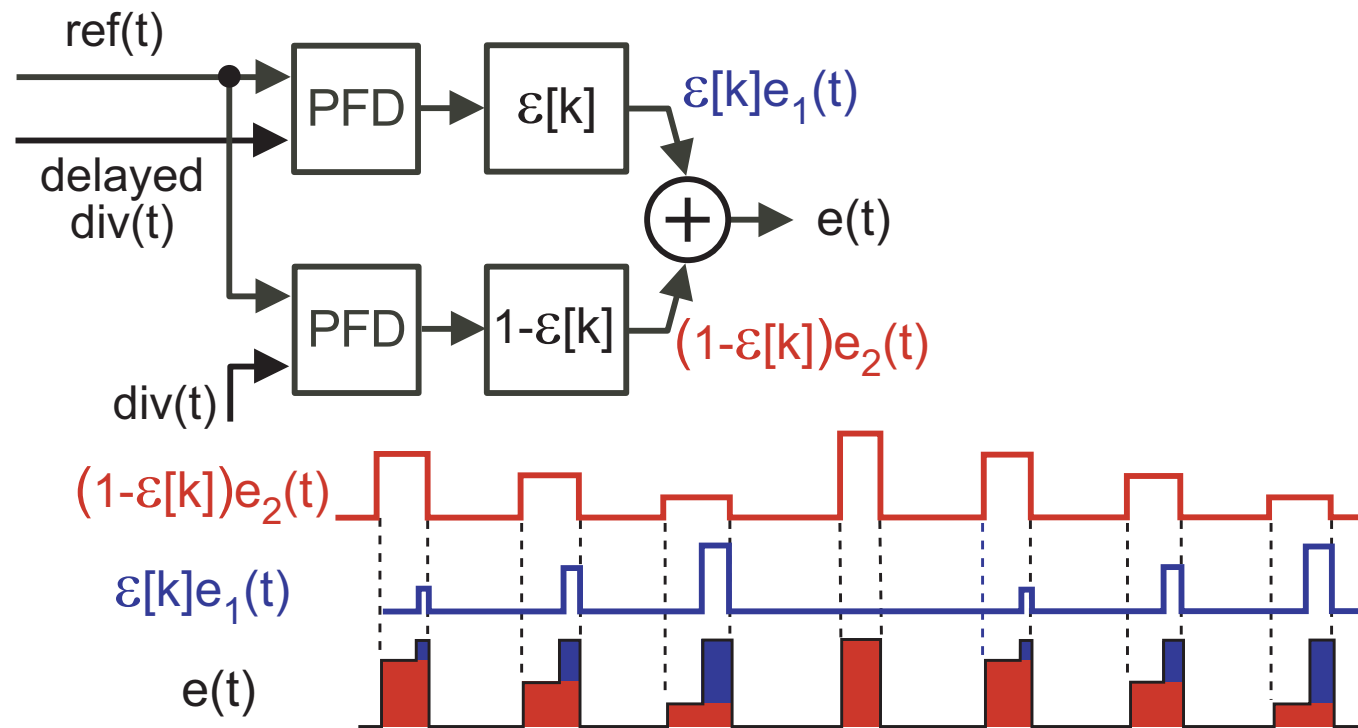
# A Closer Look at Adding the Scaled Error Pulses



- **Goal – keep area constant for each pulse**
  - It's easier to see this from a slightly different viewpoint

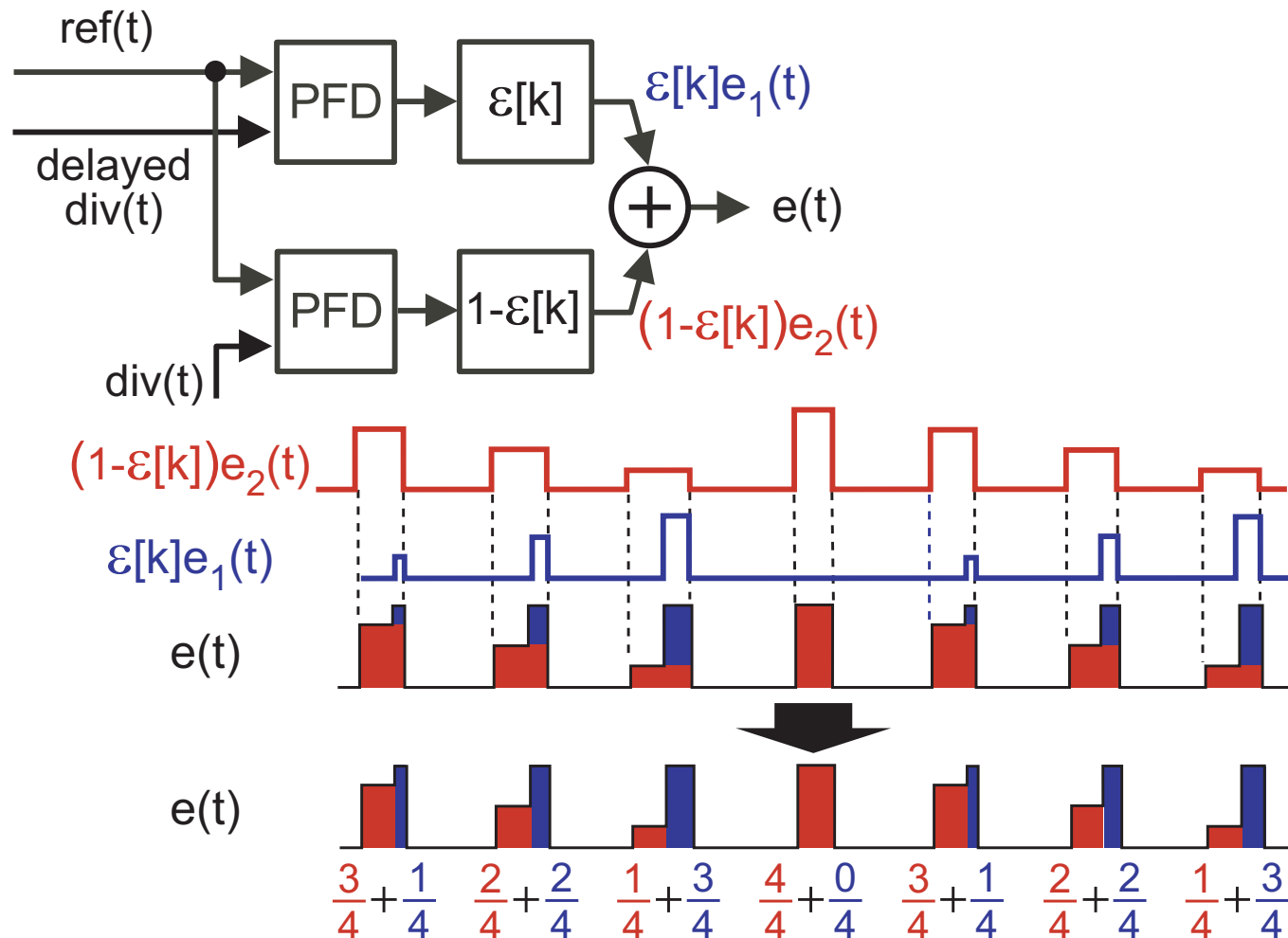
# Alternate Viewpoint

- The sum of scaled pulses can now be viewed as horizontal cancellation


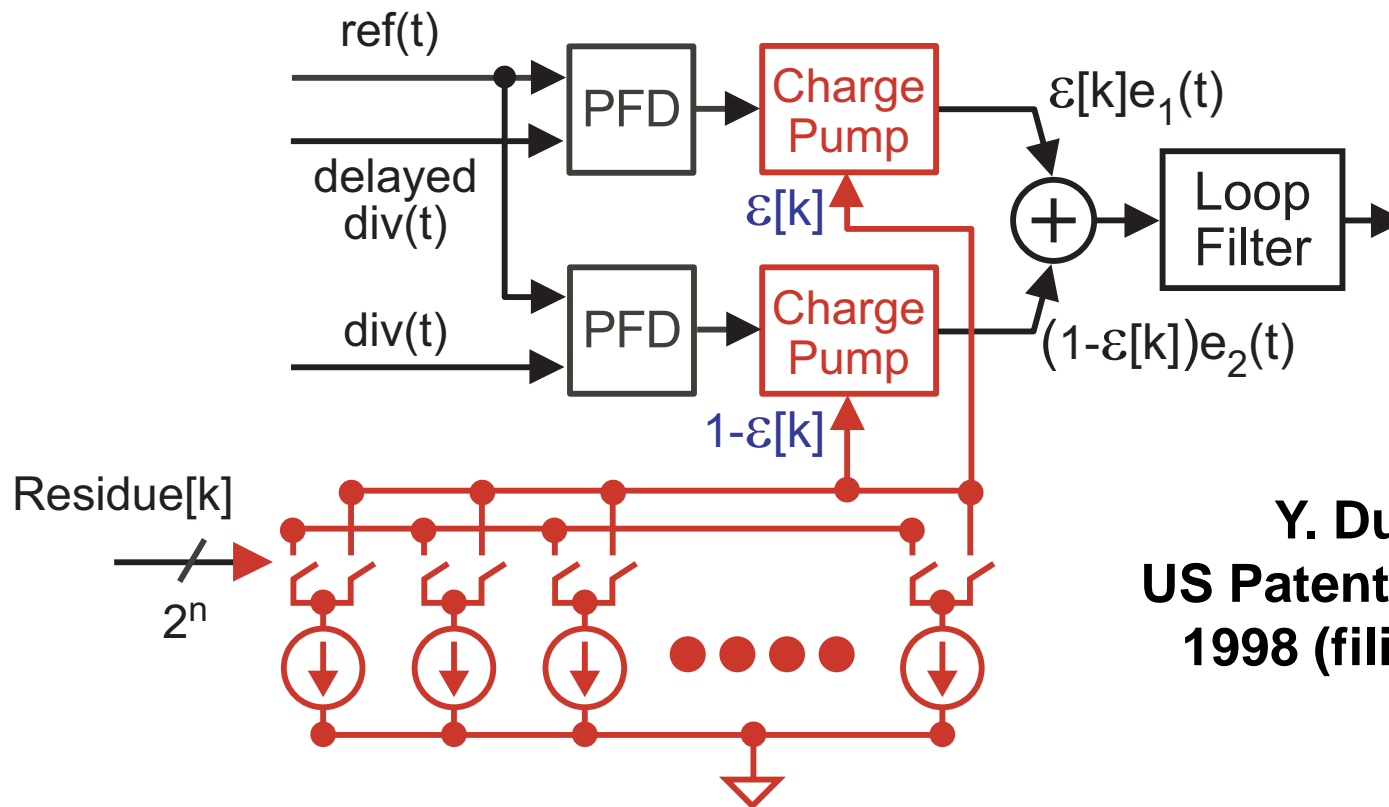
# Implementation of Pulse Scaling Operation

- Direct output of a differential current DAC into two charge pumps




- Issue: practical non-idealities kill performance

# Primary Non-idealities of Concern

**Delay mismatch**

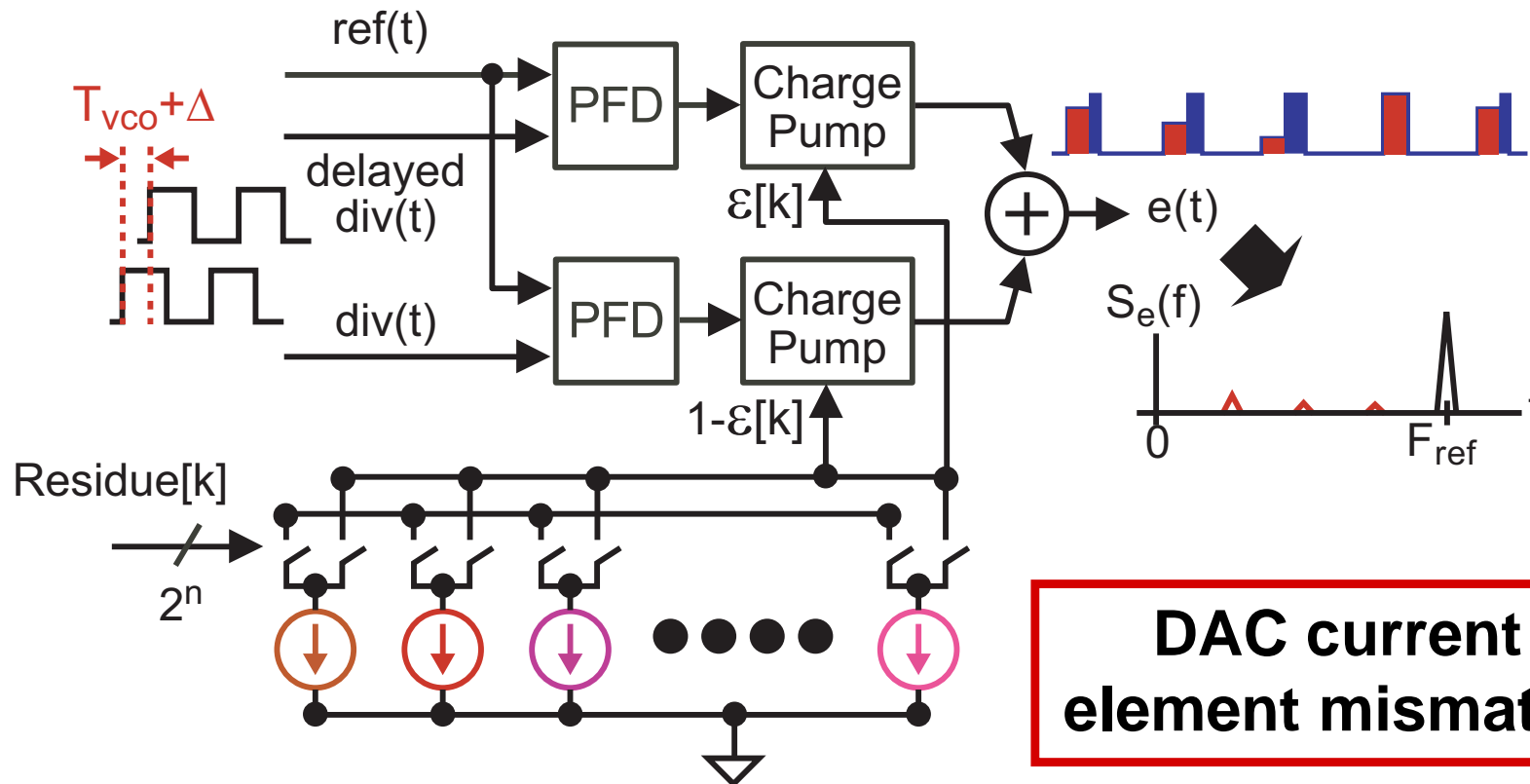**Incomplete Fractional Spur Suppression**




**DAC current element mismatch**

**Proposed approach: dramatically reduce impact of these non-idealities using mixed-signal processing techniques**
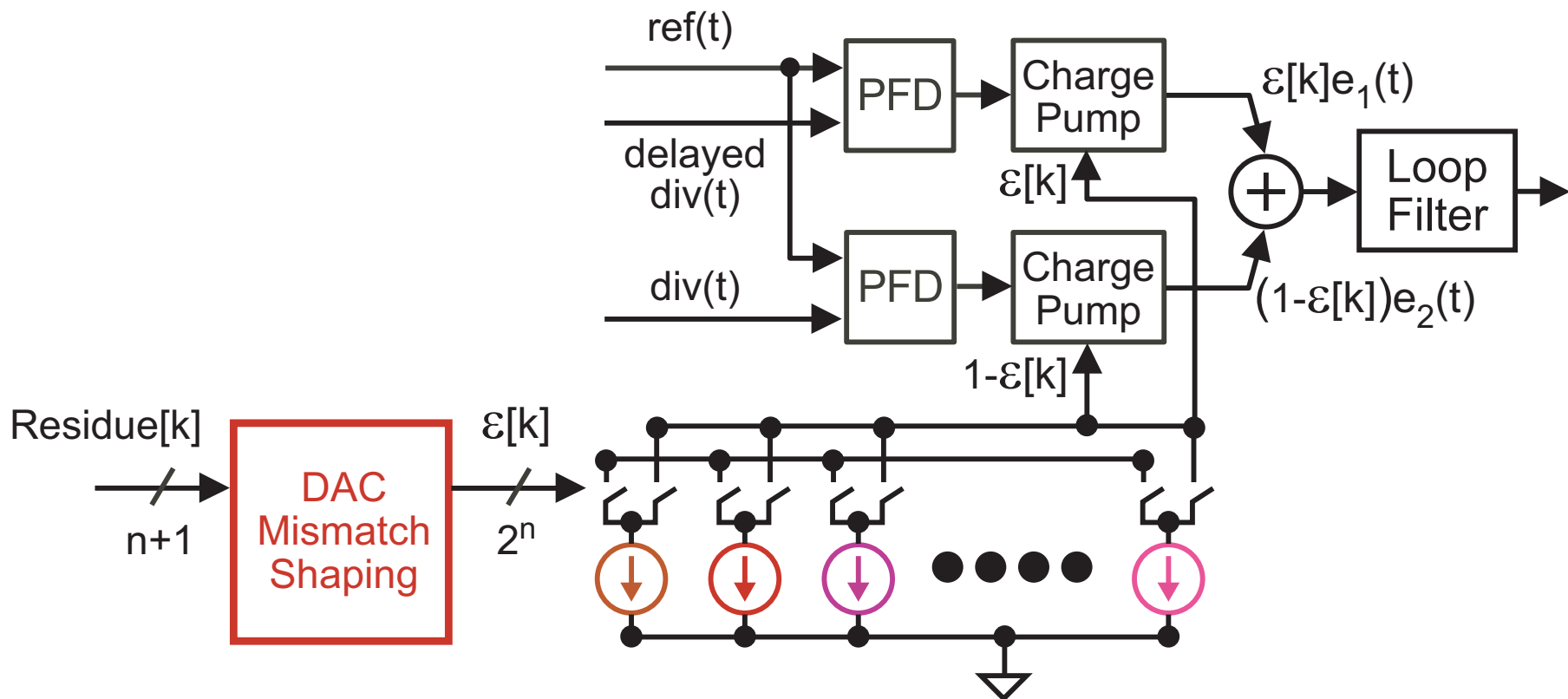
# Eliminate Impact of DAC Current Element Mismatch


- Apply standard DAC noise shaping techniques to shape mismatch noise to high frequencies
  - See Baird and Fiez, TCAS II, Dec 1995



- Allows up to 5% mismatch between unit elements without degrading our desired performance targets
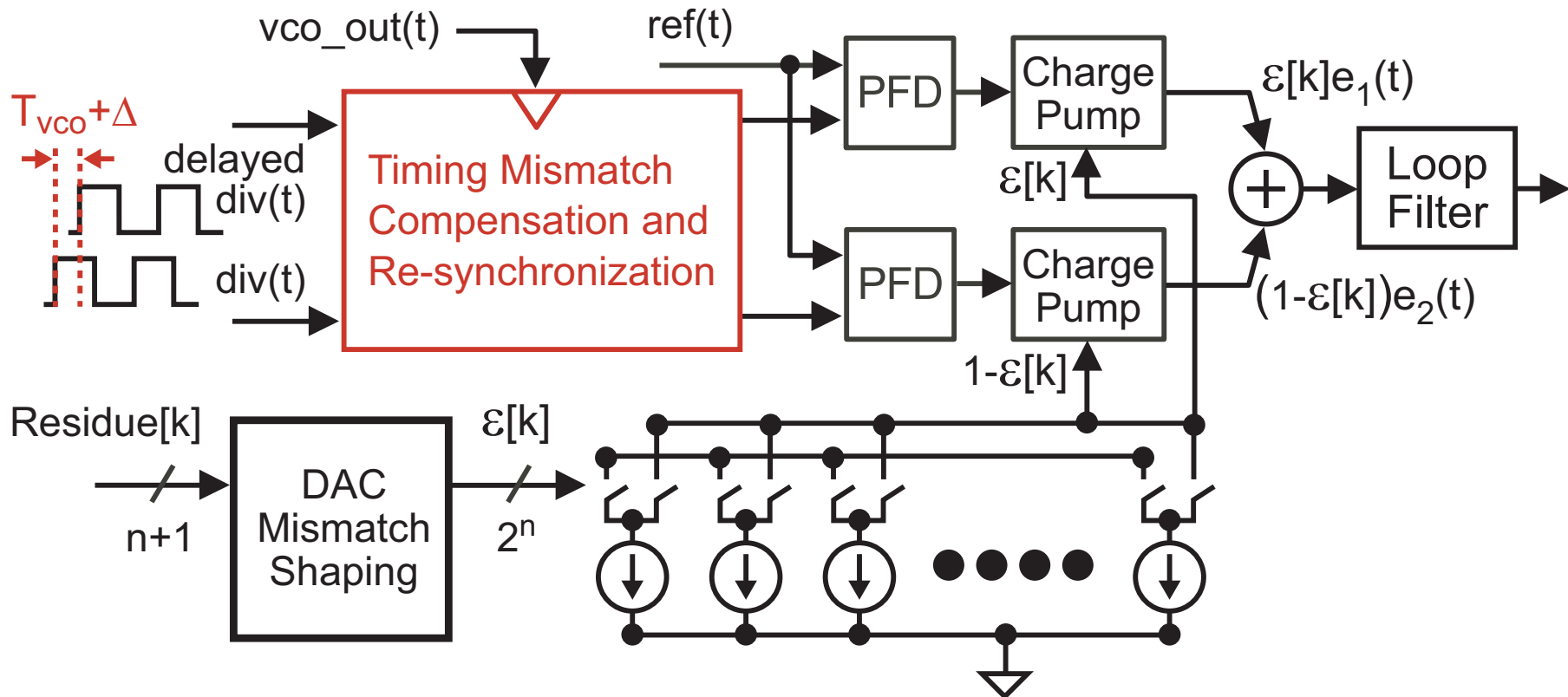
# Eliminate Impact of Timing Mismatch


- Swap paths between divider outputs in a pseudo-random fashion
  - Need to also swap  $\varepsilon[k]$  and  $1-\varepsilon[k]$  sequence



- Allows up to 5 ps mismatch without degrading our desired performance targets
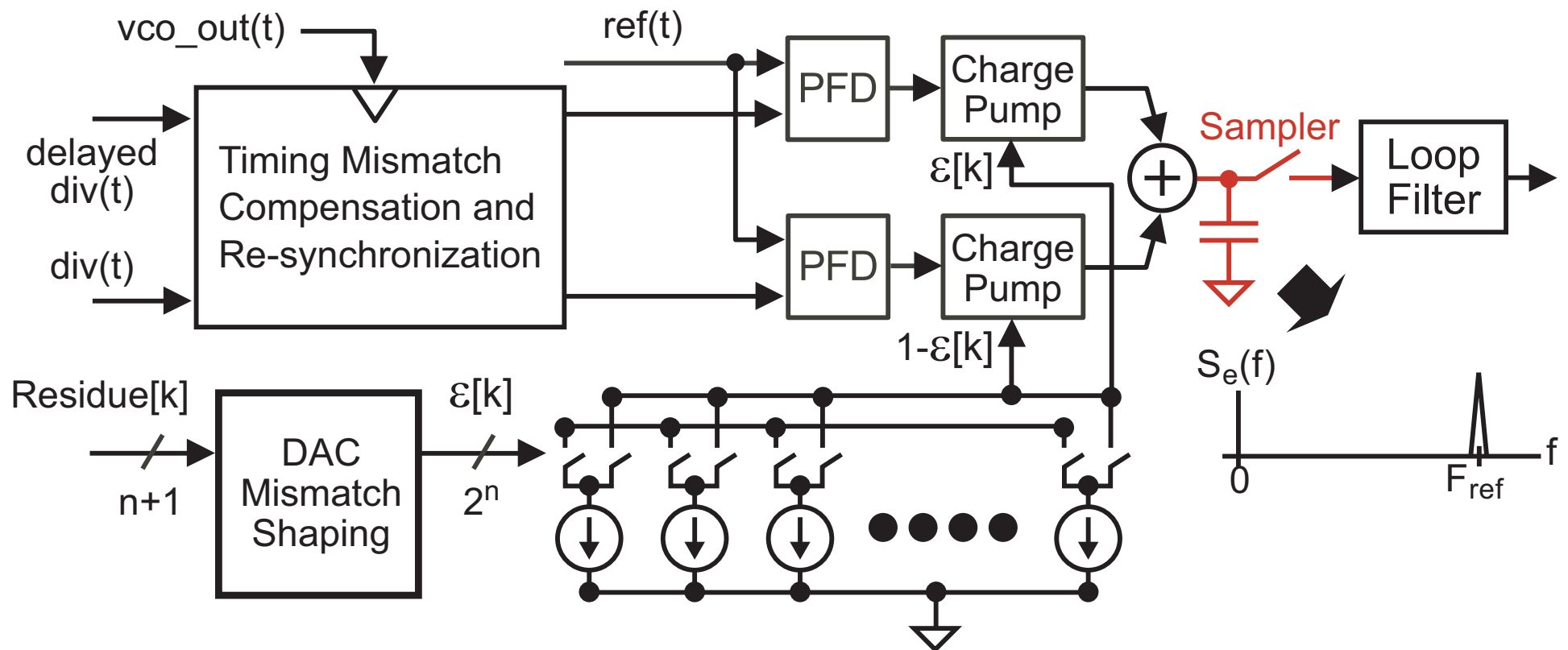
# Improve Horizontal Cancellation Performance


- Sampling circuit accumulates error pulses before passing their information to the loop filter
  - A common analog trick used for decades



- Eliminates issue of having non-square error pulse shapes

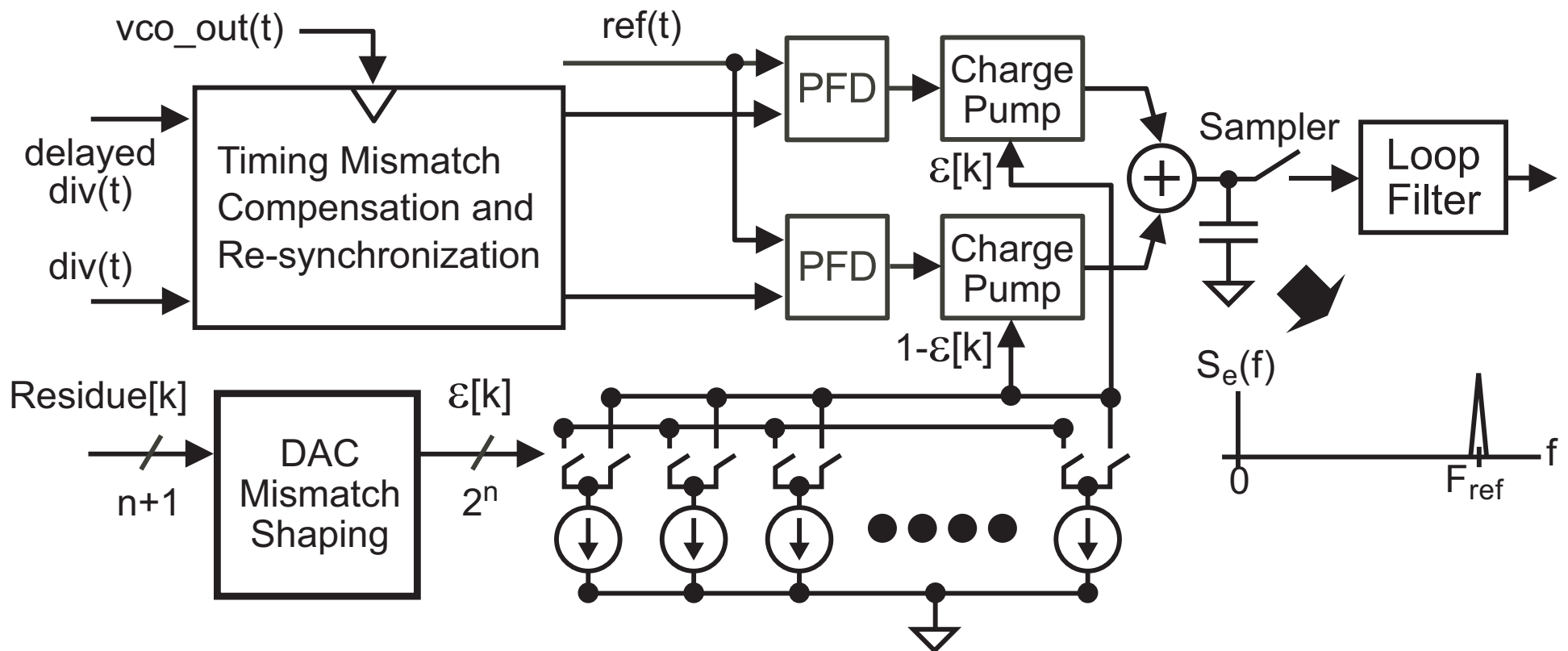
## For More Details on This Approach

- Theory and simulations presented in TCAS II paper
  - Meninger and Perrott, TCASII, Nov 2003



# ***Design and Simulation***

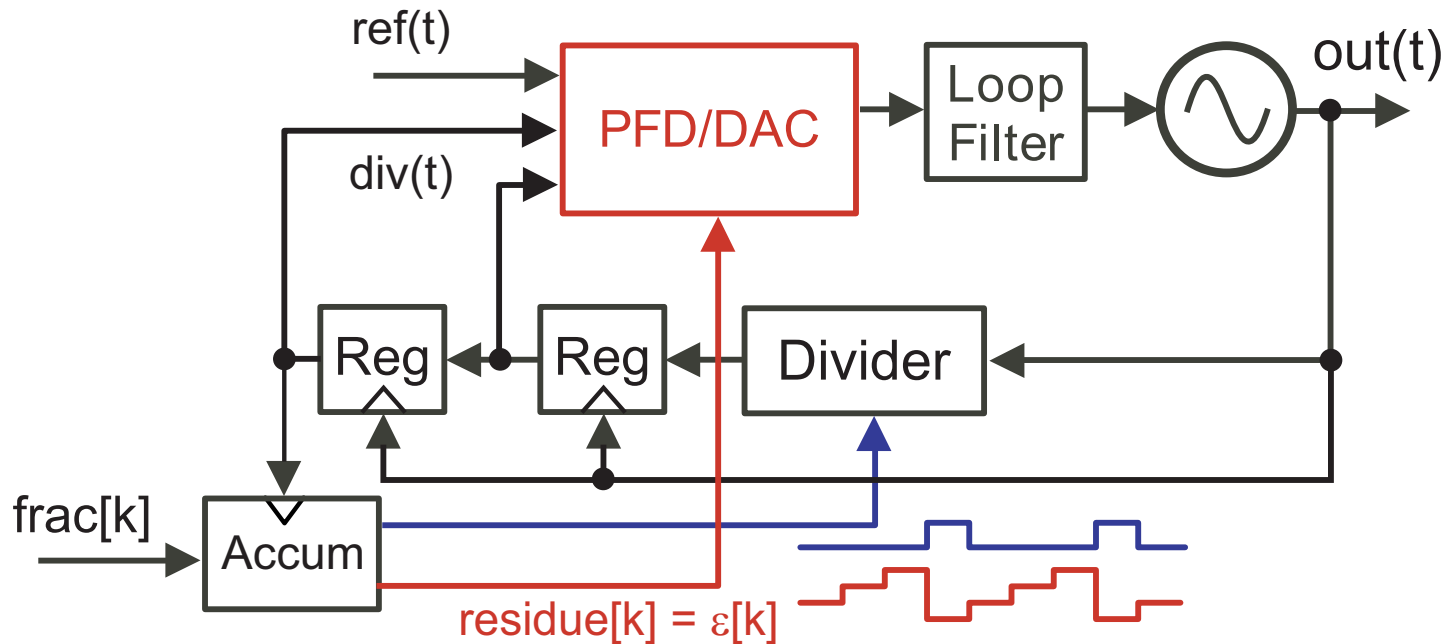
# Design and Simulation of 'PFD/DAC' Synthesizer



- **Step 1: Derive analytical model**
- **Step 2: Design at system level**
- **Step 3: Simulate at system level (CppSim)**
- **Step 4: Simulate at transistor level (SPICE)**


**Iterate between all of these steps in practice**
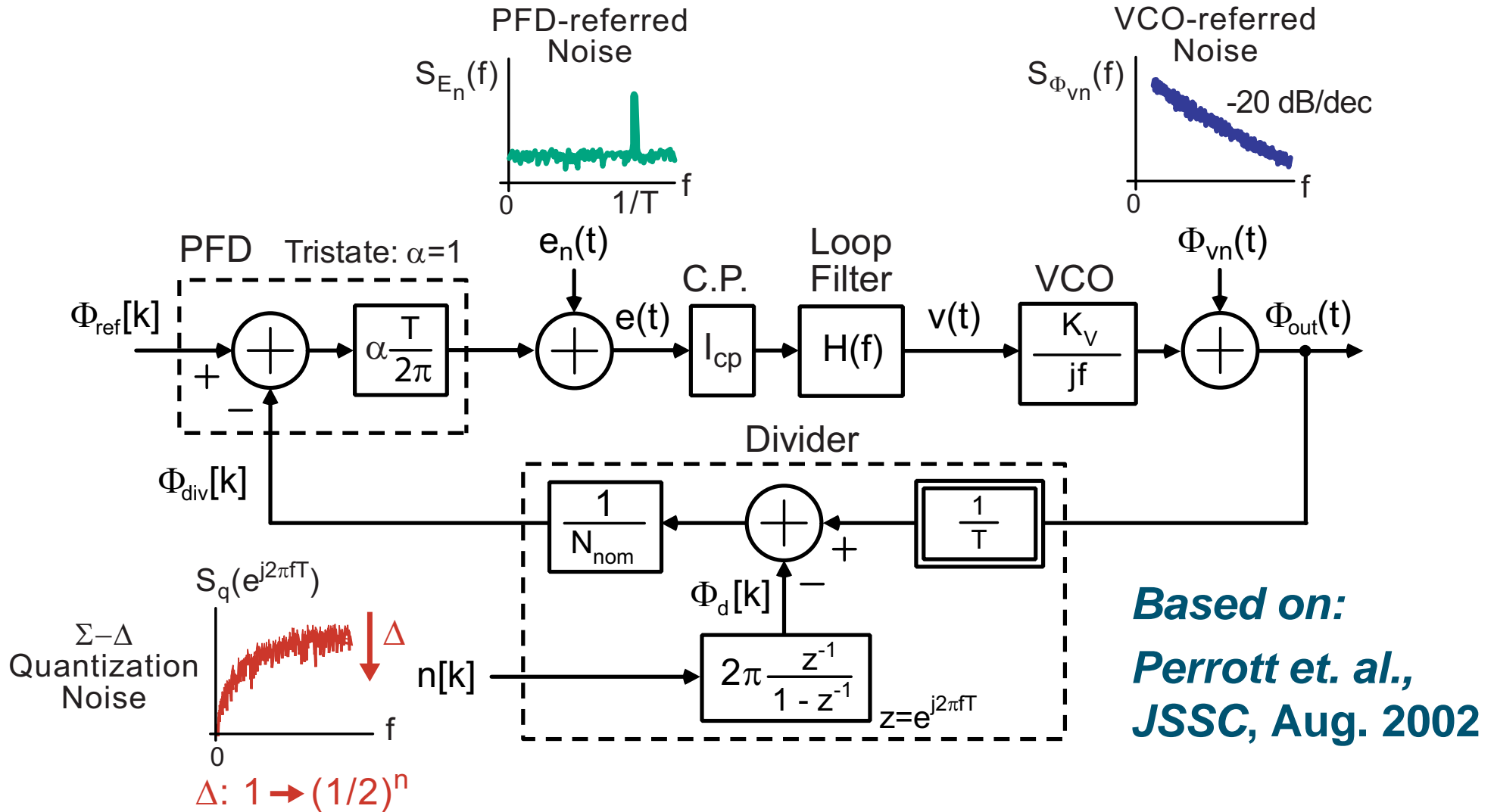
# Analytical Model of 'PFD/DAC' Fractional-N PLL



**n-bit PFD/DAC  $\rightarrow$   $\Delta$  is reduced from 1 to  $(1/2)^n$**


# Parameterized PLL Model

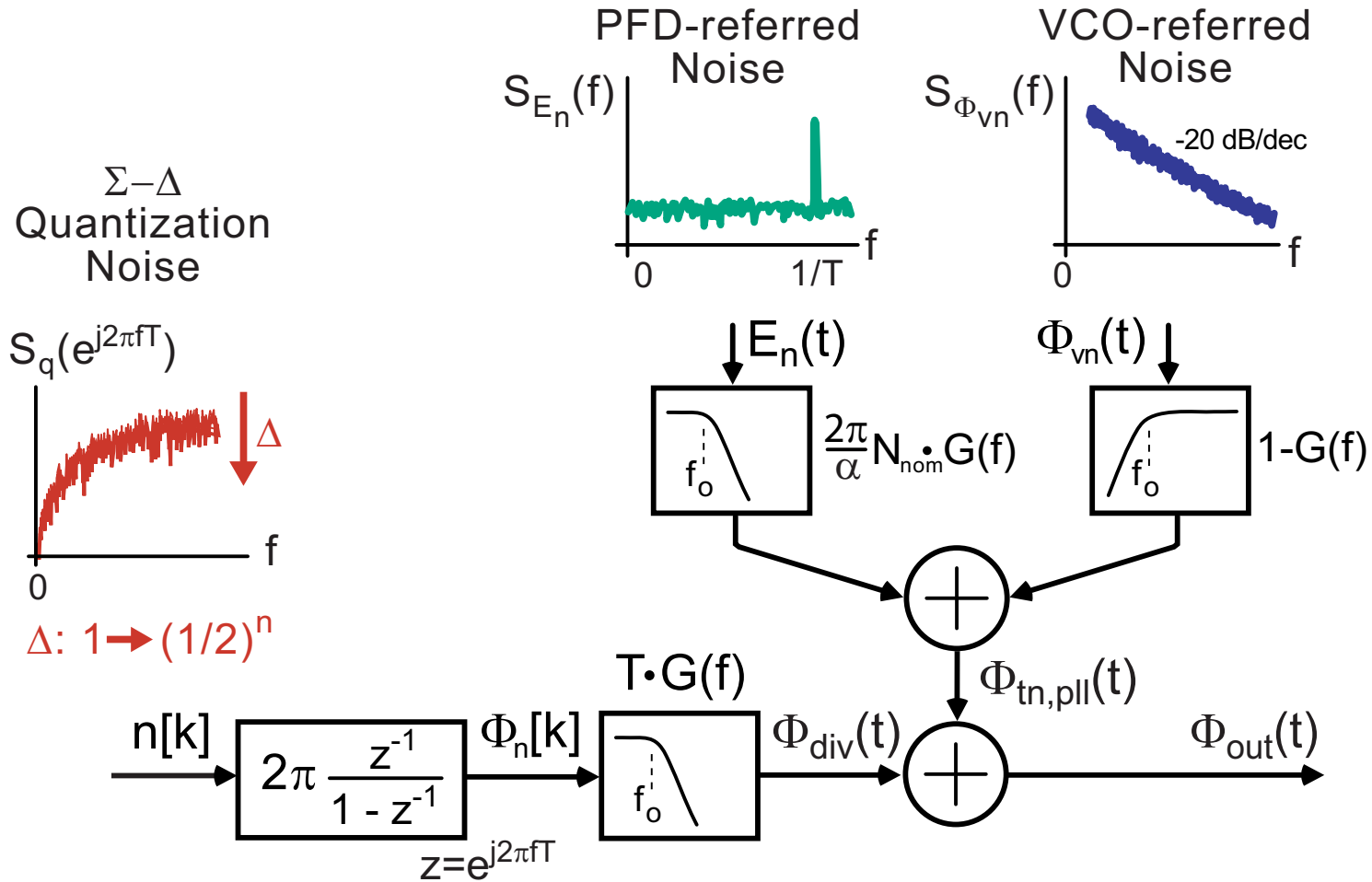

$$G(f) = \frac{A(f)}{1 + A(f)}$$

where 
$$A(f) = \frac{\alpha I_{cp} H(f) K_V}{N_{nom} 2\pi j f}$$

# Closed Loop Design Approach

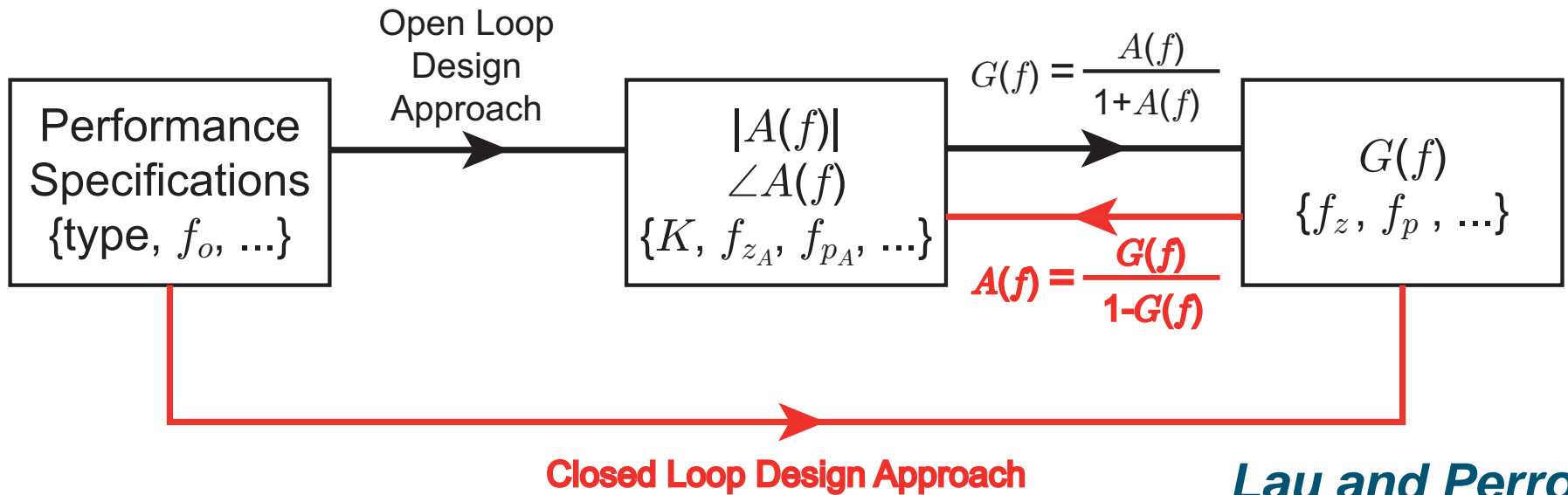


*Lau and Perrott,  
DAC, June 2003*

- **Classical approach**
  - Indirectly design  $G(f)$  using bode plots of  $A(f)$
- **Proposed approach**
  - Directly design  $G(f)$
  - Solve for  $A(f)$  that will achieve desired  $G(f)$


**Implemented in *PLL Design Assistant Software***
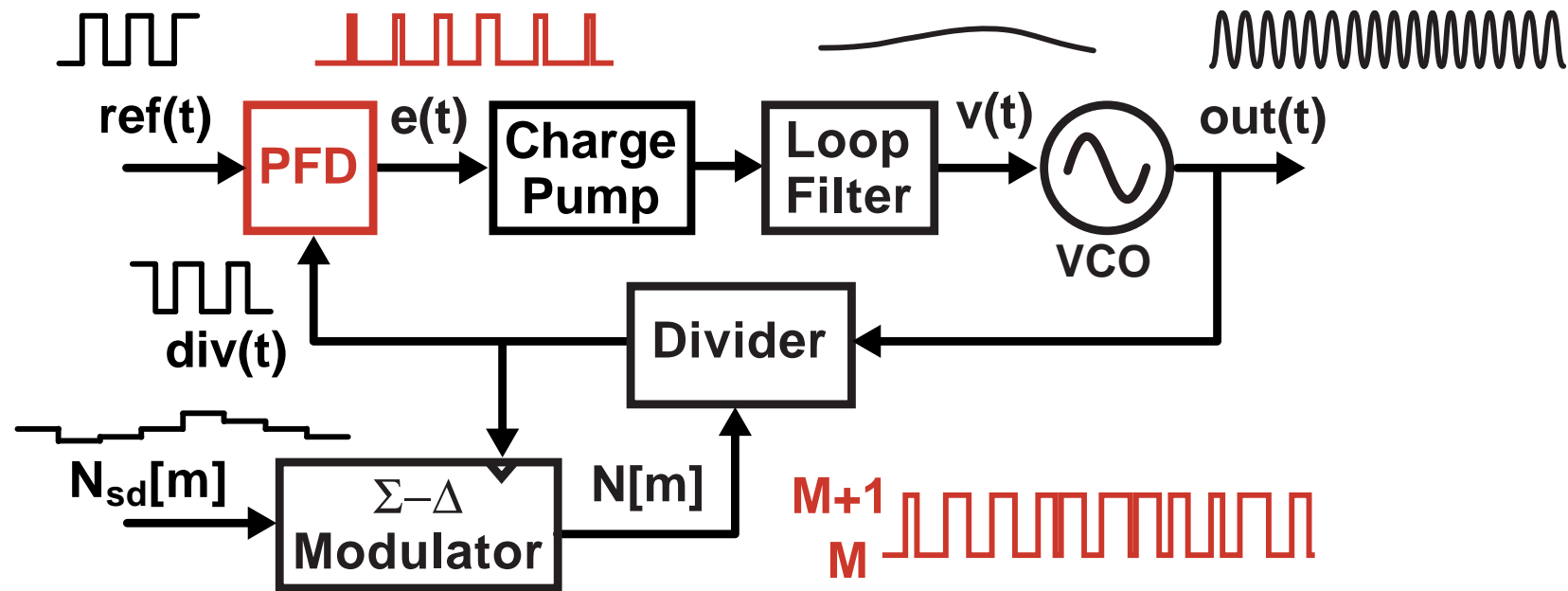
# PLL Simulation Issues (Behavioral Level)



- **Slow simulation time**
  - High output frequency  $\Rightarrow$  High sample rate
  - Long time constants  $\Rightarrow$  Long time span for transients
- **Inaccurate results**
  - PFD output information conveyed in pulses

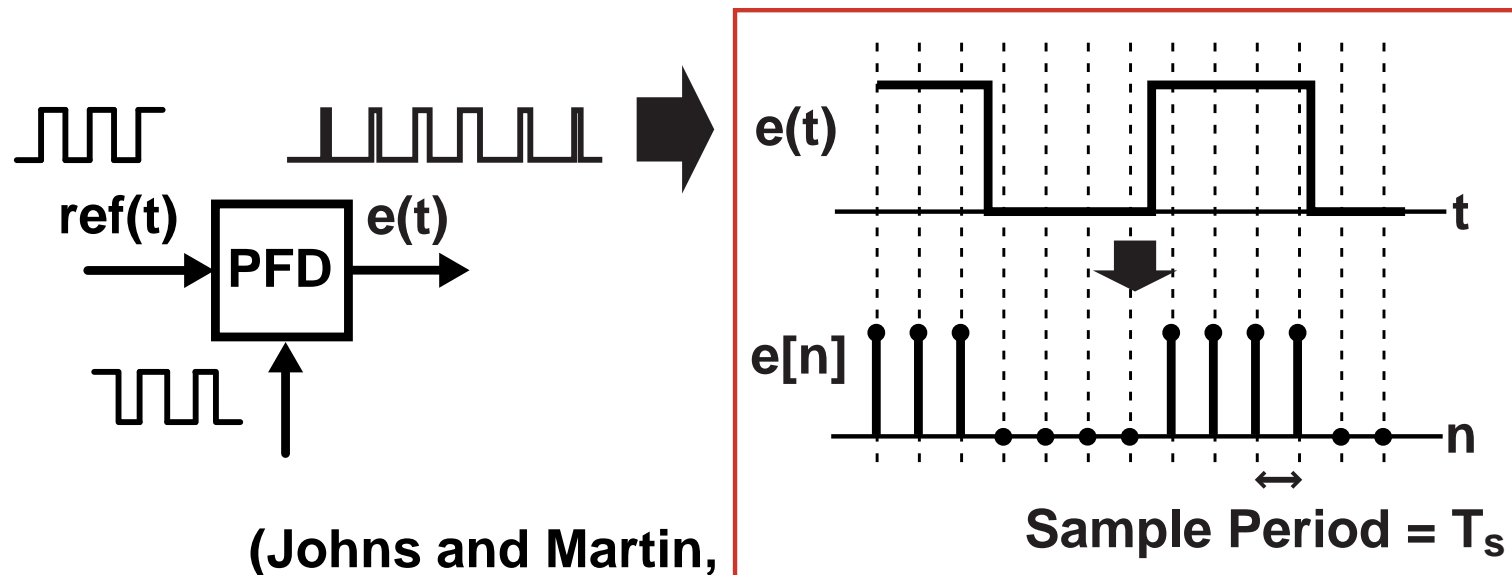
## Example: Classical Constant-Time Step Method



(Johns and Martin,  
Analog Integrated Circuit Design)


- Directly sample the PFD output according to the simulation sample period
  - Simple, fast, readily implemented in Matlab, Verilog, C++
- Issue – quantization noise is introduced
  - This noise overwhelms the PLL noise sources we are trying to simulate

## Alternative: Event Driven Simulation

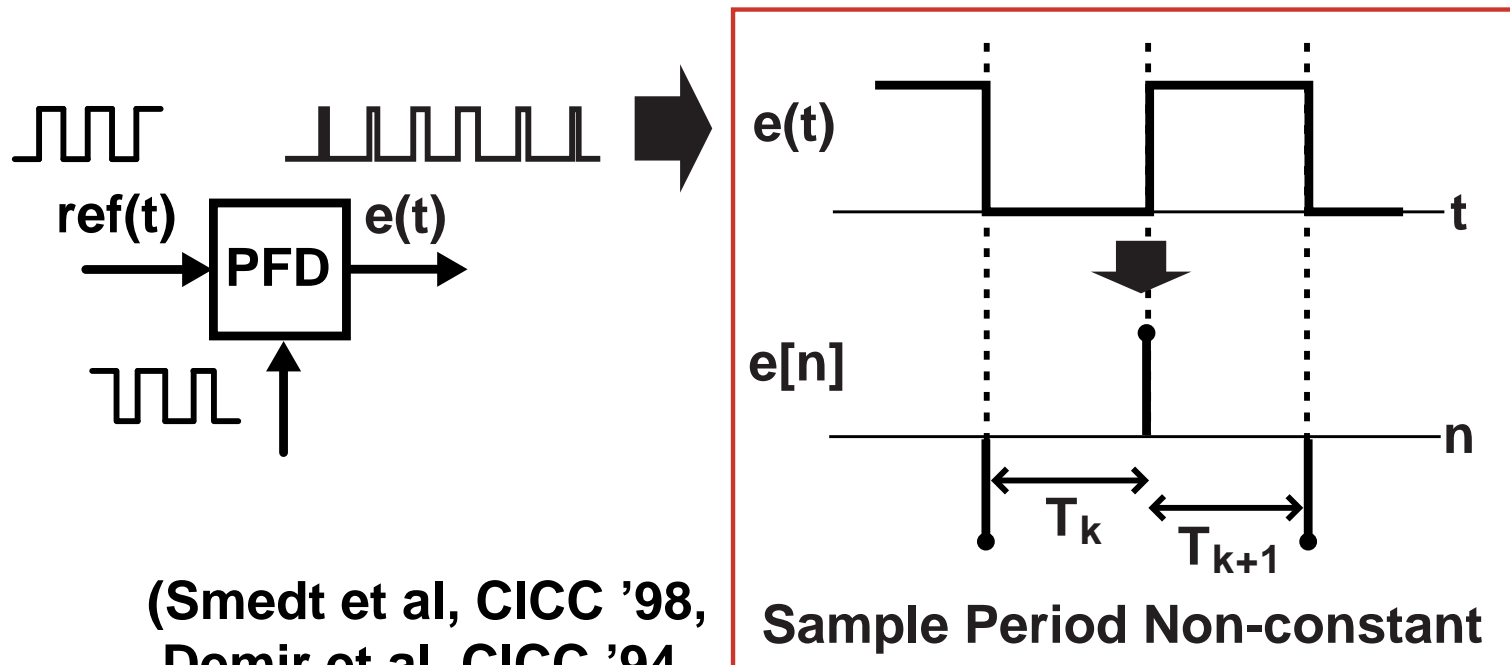

- Set simulation time samples at PFD edges
  - Sample rate can be lowered to edge rate!


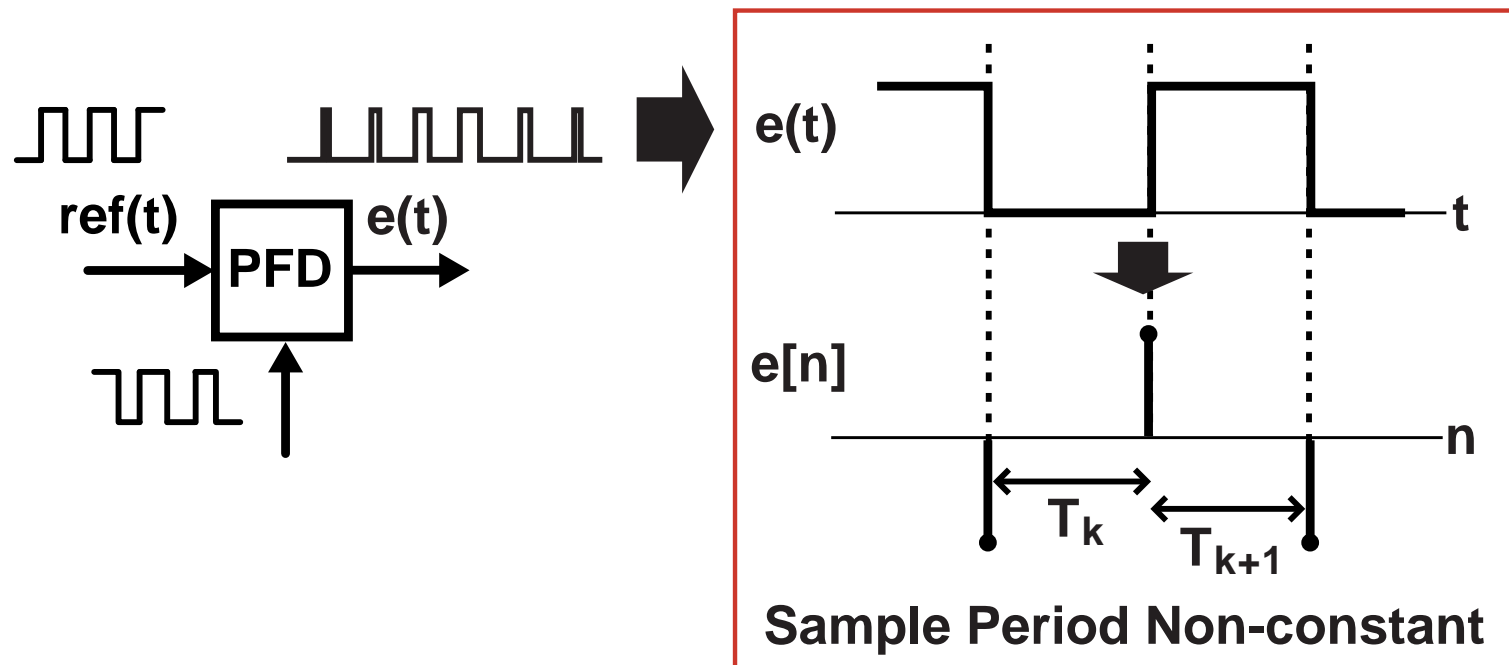
## Issue: Non-Constant Time Step Brings Complications



- Filters and noise sources must account for varying time step in their code implementations
- Spectra derived from mixing and other operations can display false simulation artifacts
- Setting of time step becomes progressively complicated if multiple PLL's simulated at once



***Is there a better way?***
  
## Problem: Quantization Noise at PFD Output




- Edge locations of PFD output are quantized
  - Resolution set by time step:  $T_s$
- Reduction of  $T_s$  leads to long simulation times
  
# Proposed Approach: View as Series of Pulses




- Area of each pulse set by edge locations
- Key observations:
  - Pulses look like impulses to loop filter
  - Impulses are parameterized by their area and time offset

# Proposed Method

 

*Perrott, DAC, June 2002*

 - Set  $e[n]$  samples according to pulse areas
  - Leads to very accurate results and fast computation
- Implemented in the CppSim Behavioral Simulator



***Application:***  
***A 1 MHz Bandwidth Fractional-N Frequency  
Synthesizer Implementation***

## *Design Goals*

---

- **Output frequency: 3.6 GHz**
  - Allows dual-band output (1.8 GHz and 900 MHz)
- **Reference frequency: 50 MHz**
  - Allows low cost crystal reference
- **Bandwidth: 1 MHz**
  - Allows fast settling time and ~1 Mbit/s modulation rate
- **Noise: < -150 dBc/Hz at 20 MHz offset (3.6 GHz carrier)**
  - Phase noise at the 20 MHz frequency offset is very challenging for GSM and DCS transmitters
    - GSM: -162 dBc/Hz at 20 MHz offset (900 MHz carrier)
    - DCS: -151 dBc/Hz at 20 MHz offset (1.8 GHz carrier)


**Simultaneous achievement of the above bandwidth and noise targets is very challenging**

## Evaluate Noise Performance with 1 MHz PLL BW


- **G(f) parameters**
  - 1 MHz BW, Type II, 2<sup>nd</sup> order rolloff, extra pole at 2.5 MHz
- **Required PLL noise parameters (with a few dB of margin)**
  - Output-referred charge pump noise: -105 dBc/Hz
  - VCO noise: -155 dBc/Hz at 20 MHz offset (3.6 GHz carrier)

Dynamic Parameters		Noise Parameters	
fo: <input type="text" value="1e6"/> Hz	paris. pole: <input type="text" value="2.5e6"/> Hz <input type="button" value="On"/>	ref. freq: <input type="text" value="50e6"/> Hz	
order: <input type="radio"/> 1 <input checked="" type="radio"/> 2 <input type="radio"/> 3	paris. Q: <input type="text"/> <input type="button" value="On"/>	out freq.: <input type="text" value="3.6e9"/> Hz	
shape: <input checked="" type="radio"/> Butter <input type="radio"/> Bessel	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	Detector: <input type="text" value="-105"/> dBc/Hz <input type="button" value="On"/>	
<input type="radio"/> Cheby1 <input type="radio"/> Cheby2 <input type="radio"/> Elliptical	paris. Q: <input type="text"/> <input type="button" value="On"/>	VCO: <input type="text" value="-155"/> dBc/Hz <input type="button" value="On"/>	
ripple: <input type="text"/> <input type="text"/> dB	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	freq. offset: <input type="text" value="20e6"/> Hz	
type: <input type="radio"/> 1 <input checked="" type="radio"/> 2	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	S-D: <input type="radio"/> 1 <input checked="" type="radio"/> 2 <input type="radio"/> 3 <input type="radio"/> 4 <input type="radio"/> 5 <input type="button" value="On"/>	<input type="button" value="On"/>
fz/fo: <input type="text" value="1/9"/>	paris. zero: <input type="text"/> Hz <input type="button" value="On"/>		
	paris. zero: <input type="text"/> Hz <input type="button" value="On"/>		
Resulting Open Loop Parameters		Resulting Plots and Jitter	
K: <input type="text" value="2.885e+012"/>	alter: <input type="text"/> <input type="button" value="On"/>	<input type="radio"/> Pole/Zero Diagram	<input type="radio"/> Transfer Function
fp: <input type="text" value="2.807e+006"/> Hz	alter: <input type="text"/> <input type="button" value="On"/>	<input type="radio"/> Step Response	<input checked="" type="radio"/> Noise Plot
fz: <input type="text" value="1.111e+005"/> Hz	alter: <input type="text"/> <input type="button" value="On"/>	<input type="text" value="10e3"/>	<input type="text" value="100e6"/>
Qp: <input type="text"/>	alter: <input type="text"/> <input type="button" value="On"/>	<input type="text" value="-170"/>	<input type="text" value="-60"/>
		rms jitter: <input type="text" value="2.197 ps"/>	
PLL Design Assistant		Written by Michael Perrott ( <a href="http://www-mtl.mit.edu/~perrott">http://www-mtl.mit.edu/~perrott</a> )	
 
# Calculated Phase Noise for Classical Fractional-N



**-132 dBc/Hz at 20 MHz**

 


**-126 dBc/Hz at 20 MHz**

**These do NOT meet  
our target of  
-150 dBc/Hz at 20 MHz  
(3.6 GHz carrier freq.)**


# Calculated Phase Noise for 7-bit PFD/DAC Synth

Dynamic Parameters		Noise Parameters	
fo	1e6 Hz	ref. freq	50e6 Hz
order	<input type="radio"/> 1 <input checked="" type="radio"/> 2 <input type="radio"/> 3	out freq.	3.6e9 Hz
shape	<input checked="" type="radio"/> Butter <input type="radio"/> Bessel	Detector	-105 dBc/Hz <input type="checkbox"/> On
ripple	<input type="text"/> dB	VCO	-155 dBc/Hz <input type="checkbox"/> On
type	<input type="radio"/> 1 <input checked="" type="radio"/> 2	freq. offset	20e6 Hz
fz/fo	1/9	S-D	<input type="radio"/> 1 <input type="radio"/> 2 <input checked="" type="radio"/> 3 <input type="radio"/> 4 <input type="radio"/> 5
paris. pole	2.5e6 Hz <input type="checkbox"/> On		<input type="checkbox"/> $[1 - 2^{-1}] * (1/2)^7$ <input type="checkbox"/> On
paris. Q	<input type="text"/> <input type="checkbox"/> On	<b>Resulting Plots and Jitter</b>	
paris. pole	<input type="text"/> Hz <input type="checkbox"/> On	<input type="radio"/> Pole/Zero Diagram	<input type="radio"/> Transfer Function
paris. Q	<input type="text"/> <input type="checkbox"/> On	<input type="radio"/> Step Response	<input checked="" type="radio"/> Noise Plot
paris. pole	<input type="text"/> Hz <input type="checkbox"/> On	10e3	100e6
paris. pole	<input type="text"/> Hz <input type="checkbox"/> On	-170	-60
paris. zero	<input type="text"/> Hz <input type="checkbox"/> On	rms jitter:	431.497 fs
paris. zero	<input type="text"/> Hz <input type="checkbox"/> On	by Michael Perrott ( <a href="http://www-mtl.mit.edu/~perrott">http://www-mtl.mit.edu/~perrott</a> )	

 

**-155 dBc/Hz at 20 MHz !**
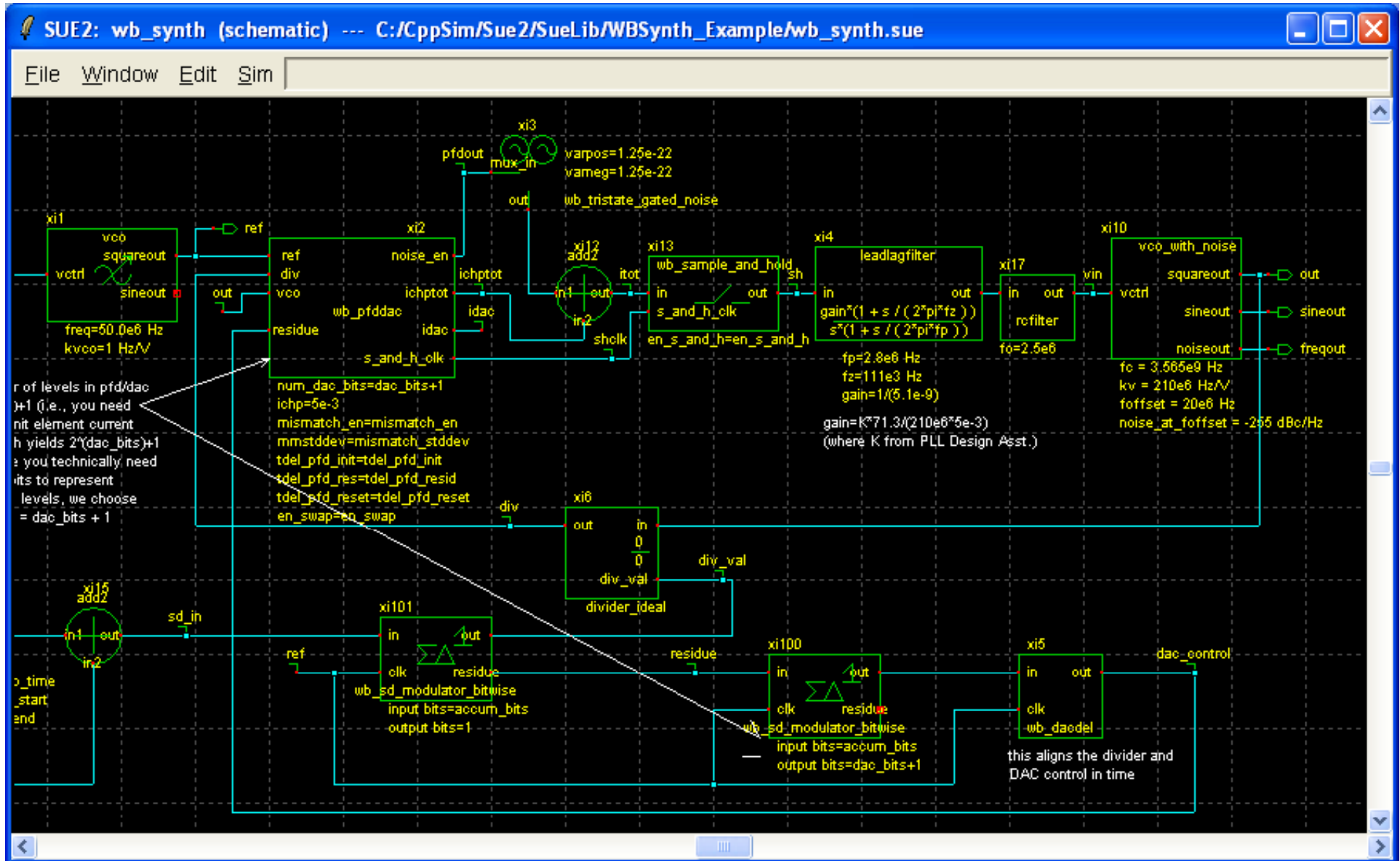
# Simulation of PFD/DAC Synthesizer using CppSim



- Phase noise plots to follow: 40e6 time steps, < 15 min



# Calculate Intrinsic PLL Noise Sources

---

- **Estimate detector noise (dominated by charge pump)**
  - From SPICE Simulation,  $S_{I_{cp}}(f) = \text{Duty} \cdot 1.25 \cdot 10^{-22} \text{ A}^2/\text{Hz}$
  - Output-referred PLL noise due to above noise:

$$\begin{aligned} S_{\Phi_{out}}(f) &= \left(\frac{1}{I_{cp}}\right)^2 \left(\frac{2\pi}{\alpha} N_{nom}\right)^2 |G(f)|^2 S_{I_{cp}}(f) \\ &= \left(\frac{1}{5 \cdot 10^{-3}}\right)^2 \left(\frac{2\pi}{1} 71.3\right)^2 |G(f)|^2 0.2 \cdot 1.25 \cdot 10^{-22} \end{aligned}$$

$$\implies 10 \log(S_{\Phi_{out}}(f)) = -127 |G(f)|^2 \text{ dBc/Hz}$$


- **Estimate VCO noise**
  - For off-chip VCO, examine data sheet:
    - In this case,  $S_{\Phi_{VCO}} = -155 \text{ dBc/Hz}$  at 20 MHz offset
  - For on-chip VCO, use Spectre RF or other CAD tool

# Calculate PLL Noise Due to Intrinsic Noise Sources

Dynamic Parameters		Noise Parameters	
fo: <input type="text" value="1e6"/> Hz	ref. freq: <input type="text" value="50e6"/> Hz	out freq.: <input type="text" value="3.6e9"/> Hz	Detector: <input type="text" value="-127"/> dBc/Hz <input type="button" value="On"/>
order: <input type="radio"/> 1 <input checked="" type="radio"/> 2 <input type="radio"/> 3	paris. pole: <input type="text" value="2.5e6"/> Hz <input type="button" value="On"/>	freq. offset: <input type="text" value="20e6"/> Hz	VCO: <input type="text" value="-155"/> dBc/Hz <input type="button" value="On"/>
shape: <input checked="" type="radio"/> Butter <input type="radio"/> Bessel	paris. Q: <input type="text"/>	S-D: <input type="radio"/> 1 <input type="radio"/> 2 <input type="radio"/> 3 <input type="radio"/> 4 <input type="radio"/> 5	<input type="button" value="On"/>
<input type="radio"/> Cheby1 <input type="radio"/> Cheby2 <input type="radio"/> Elliptical	paris. pole: <input type="text"/>		
ripple: <input type="text"/> dB	paris. Q: <input type="text"/>		
type: <input type="radio"/> 1 <input checked="" type="radio"/> 2	paris. pole: <input type="text"/>		
fz/fo: <input type="text" value="1/9"/>	paris. pole: <input type="text"/>		
	paris. zero: <input type="text"/>		
	paris. zero: <input type="text"/>		


Resulting Plots and Jitter			
<input type="radio"/> Pole/Zero Diagram	<input type="radio"/> Transfer Function	<input type="radio"/> Step Response	<input checked="" type="radio"/> Noise Plot
<input type="text" value="10e3"/>	<input type="text" value="100e6"/>	<input type="text" value="-170"/>	<input type="text" value="-60"/>
rms jitter: <b>56.456 fs</b>			
Michael Perrott ( <a href="http://www-mtl.mit.edu/~perrott">http://www-mtl.mit.edu/~perrott</a> )			

 

- We will see that we will need to include:
  - Excess noise
  - 1/f noise

 
# Simulated Phase Noise due to Intrinsic Noise Sources

>ppSim Simulated Phase Noise for Cell: wb\_synth, Lib: WBSynth\_Example, Sim: test\_int\_n.par



- PLL Design Assistant accurately models simulated noise!
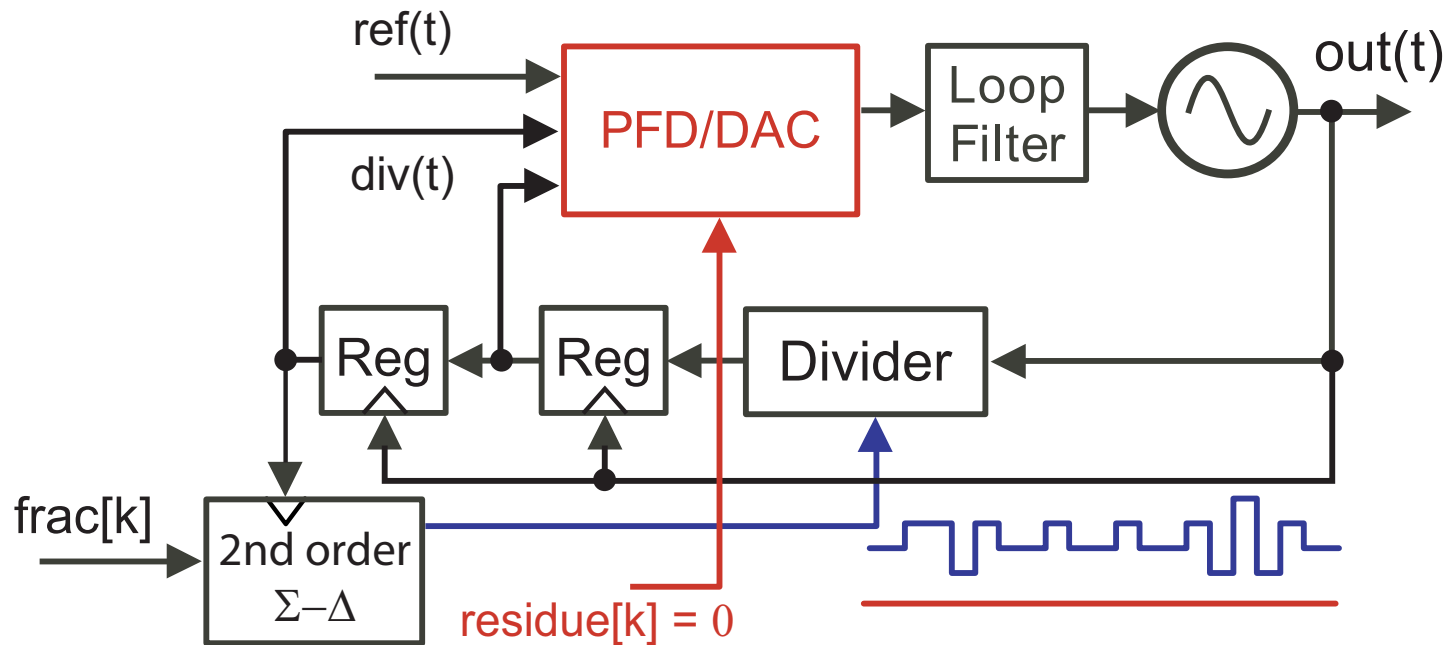
## 2<sup>nd</sup> Order $\Sigma\text{-}\Delta$ Fractional-N Performance



- Replace accumulator with second order  $\Sigma\text{-}\Delta$  modulator
- Set residue into PFD/DAC equal to zero

# Calculate PLL Noise for 2<sup>nd</sup> Order $\Sigma$ - $\Delta$ Synthesizer

Dynamic Parameters		Noise Parameters	
fo	1e6 Hz	ref. freq	50e6 Hz
order	<input type="radio"/> 1 <input checked="" type="radio"/> 2 <input type="radio"/> 3	out freq.	3.6e9 Hz
shape	<input checked="" type="radio"/> Butter <input type="radio"/> Bessel	Detector	-127 dBc/Hz <input type="checkbox"/> On
	<input type="radio"/> Cheby1 <input type="radio"/> Cheby2 <input type="radio"/> Elliptical	VCO	-155 dBc/Hz <input type="checkbox"/> On
ripple	dB	freq. offset	20e6 Hz
type	<input type="radio"/> 1 <input checked="" type="radio"/> 2	S-D	<input type="radio"/> 1 <input checked="" type="radio"/> 2 <input type="radio"/> 3 <input type="radio"/> 4 <input type="radio"/> 5 <input type="checkbox"/> On
fz/fo	1/9		
paris. pole	2.5e6 Hz <input type="checkbox"/> On		
paris. Q	<input type="checkbox"/> On		
paris. pole	Hz <input type="checkbox"/> On		
paris. Q	<input type="checkbox"/> On		
paris. pole	Hz <input type="checkbox"/> On		
paris. pole	Hz <input type="checkbox"/> On		
paris. zero	Hz <input type="checkbox"/> On		
paris. zero	Hz <input type="checkbox"/> On		


**Resulting Plots and Jitter**

Pole/Zero Diagram     Transfer Function  
 Step Response     Noise Plot

10e3    100e6    -170    -60

rms jitter: **2.155 ps**

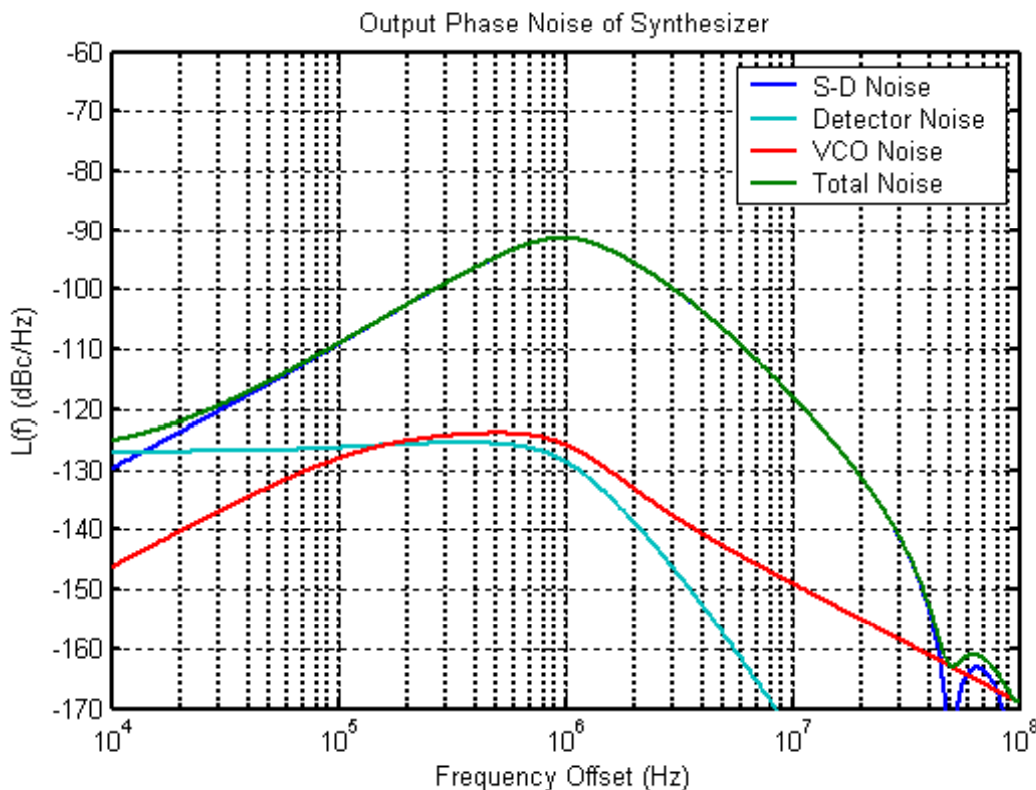
by Michael Perrott (<http://www-mtl.mit.edu/~perrott>)



- 2<sup>nd</sup> order  $\Sigma$ - $\Delta$
- Click on 2<sup>nd</sup> order S-D quantization noise in tool
 
# Simulated Phase Noise of 2<sup>nd</sup> Order $\Sigma$ - $\Delta$ Synthesizer


CppSim Simulated Phase Noise for Cell: wb\_synth\_sd2, Lib: WBSynth\_Example, Sim: test.par



- **PLL Design Assistant accurately models simulated noise!**

# 7-bit PFD/DAC Synthesizer Performance

## Delay mismatch

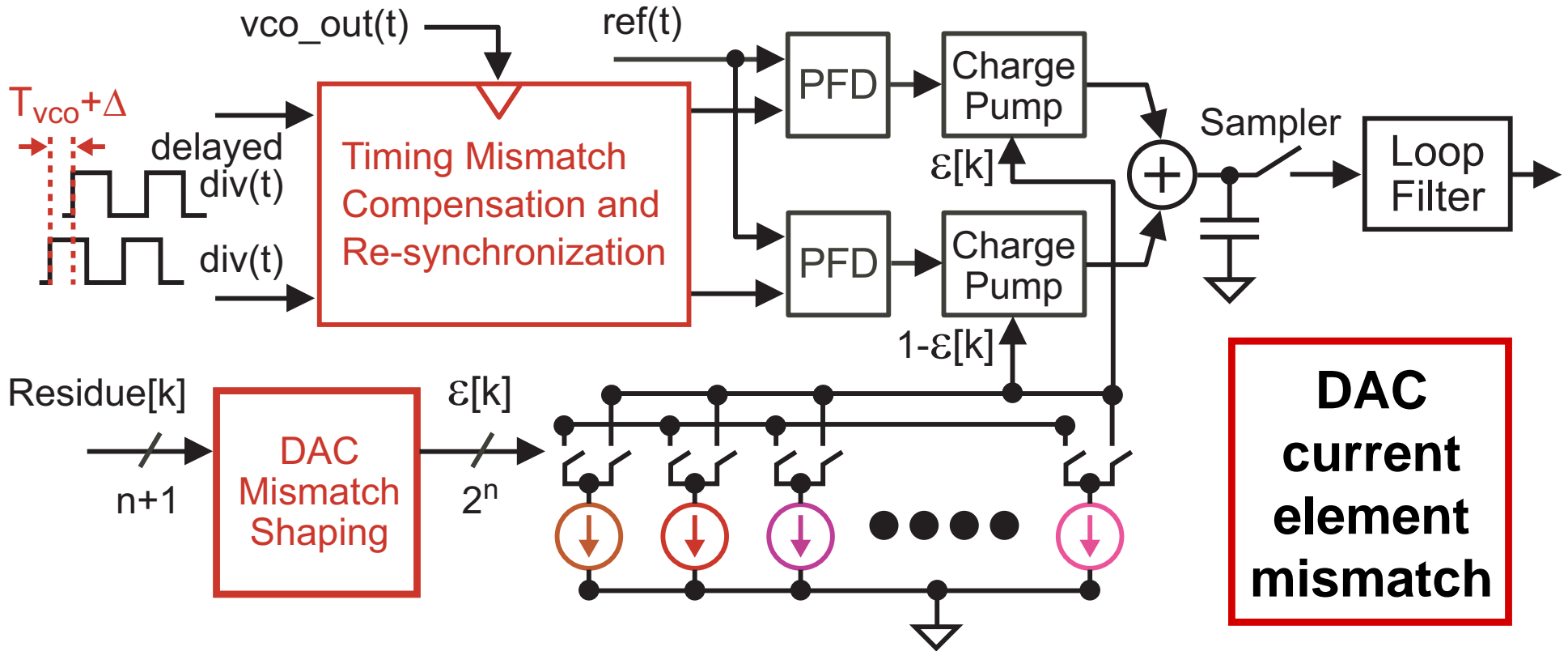

Application of proposed noise scrambling/shaping techniques leads to broadband noise from delay and DAC current mismatch

# Impact on PLL Noise due to Non-idealities of PFD/DAC

- Impact of DAC mismatch
  - Lowers achievable quantization noise suppression
  - Negligible in this case
- Impact of delay mismatch
  - Model as white reference noise uniformly distributed from 0 to  $\Delta t$ 
    - Calculation for  $\Delta t = 5$  ps:

$$\begin{aligned} S_{\Phi_{out}}(f) &= \frac{1}{T} |TN_{nom}G(f)|^2 S_{\Phi_{jit}}(e^{j2\pi fT}) \\ &= \frac{1}{T} |TN_{nom}G(f)|^2 \left| \frac{2\pi}{T} \right|^2 \frac{(\Delta t)^2}{12} \\ &= (50 \text{ MHz})(71.3)^2 (2\pi)^2 \frac{(5\text{ps})^2}{12} \end{aligned}$$


$$\implies 10 \log(S_{\Phi_{out}}(f)) = -107 |G(f)|^2 \text{ dBc/Hz}$$

# Calculate PLL Noise for 7-bit PFD/DAC Synthesizer

Dynamic Parameters		Noise Parameters	
fo	1e6 Hz	ref. freq	50e6 Hz
order	<input type="radio"/> 1 <input checked="" type="radio"/> 2 <input type="radio"/> 3	out freq.	3.6e9 Hz
shape	<input checked="" type="radio"/> Butter <input type="radio"/> Bessel	Detector	-107 dBc/Hz <input type="checkbox"/> On
	<input type="radio"/> Cheby1 <input type="radio"/> Cheby2 <input type="radio"/> Elliptical	VCO	-155 dBc/Hz <input type="checkbox"/> On
ripple	dB	freq. offset	20e6 Hz
type	<input type="radio"/> 1 <input checked="" type="radio"/> 2	S-D	<input type="radio"/> 1 <input type="radio"/> 2 <input checked="" type="radio"/> 3 <input type="radio"/> 4 <input type="radio"/> 5
fz/fo	1/9		<input type="checkbox"/> On <input type="checkbox"/> On
paris. pole	2.5e6 Hz <input type="checkbox"/> On		<input type="checkbox"/> On <input type="checkbox"/> On
paris. Q	<input type="checkbox"/> On		<input type="checkbox"/> On <input type="checkbox"/> On
paris. pole	Hz <input type="checkbox"/> On		<input type="checkbox"/> On <input type="checkbox"/> On
paris. Q	<input type="checkbox"/> On		<input type="checkbox"/> On <input type="checkbox"/> On
paris. pole	Hz <input type="checkbox"/> On		<input type="checkbox"/> On <input type="checkbox"/> On
paris. pole	Hz <input type="checkbox"/> On		<input type="checkbox"/> On <input type="checkbox"/> On
paris. zero	Hz <input type="checkbox"/> On		<input type="checkbox"/> On <input type="checkbox"/> On
paris. zero	Hz <input type="checkbox"/> On		<input type="checkbox"/> On <input type="checkbox"/> On


Resulting Plots and Jitter	
<input type="radio"/> Pole/Zero Diagram	<input type="radio"/> Transfer Function
<input type="radio"/> Step Response	<input checked="" type="radio"/> Noise Plot
10e3	100e6
-170	-60
rms jitter:	343.992 fs
by Michael Perrott ( <a href="http://www-mtl.mit.edu/~perrott">http://www-mtl.mit.edu/~perrott</a> )	

 

- **PFD/DAC**
  - Adjust S-D Quant. Noise
- **Delay mismatch**
  - Adjust Detector noise
 
# Simulated PLL Phase Noise of 7-bit PFD/DAC

CppSim Simulated Phase Noise for Cell: wb\_synth, Lib: WBSynth\_Example, Sim: test.par



- PLL Design Assistant accurately models simulated noise!

## ***Summary of Design/Simulation Results***


---

- **The PLL Design Assistant can be used to model the impact of**
  - **Intrinsic PLL noise sources**
  - **Quantization noise due to  $\Sigma-\Delta$  dithering of divide value**
  - **Suppression of quantization noise by n-bit PFD/DAC**
  - **Impact of delay and current mismatch on PLL phase noise**
- **CppSim simulations confirm the accuracy of the above analysis**

**How do PLL Design Assistant calculations compare to measured results?**

# A 1 MHz BW Fractional-N Frequency Synthesizer IC

**Scott Meninger**

 


- Implements proposed 7-bit PFD/DAC structure
  - 0.18u CMOS
  - Circuit details to be published in the future

**Funded by  
MARCO C2S2**


**Fabricated by  
National  
Semiconductor**
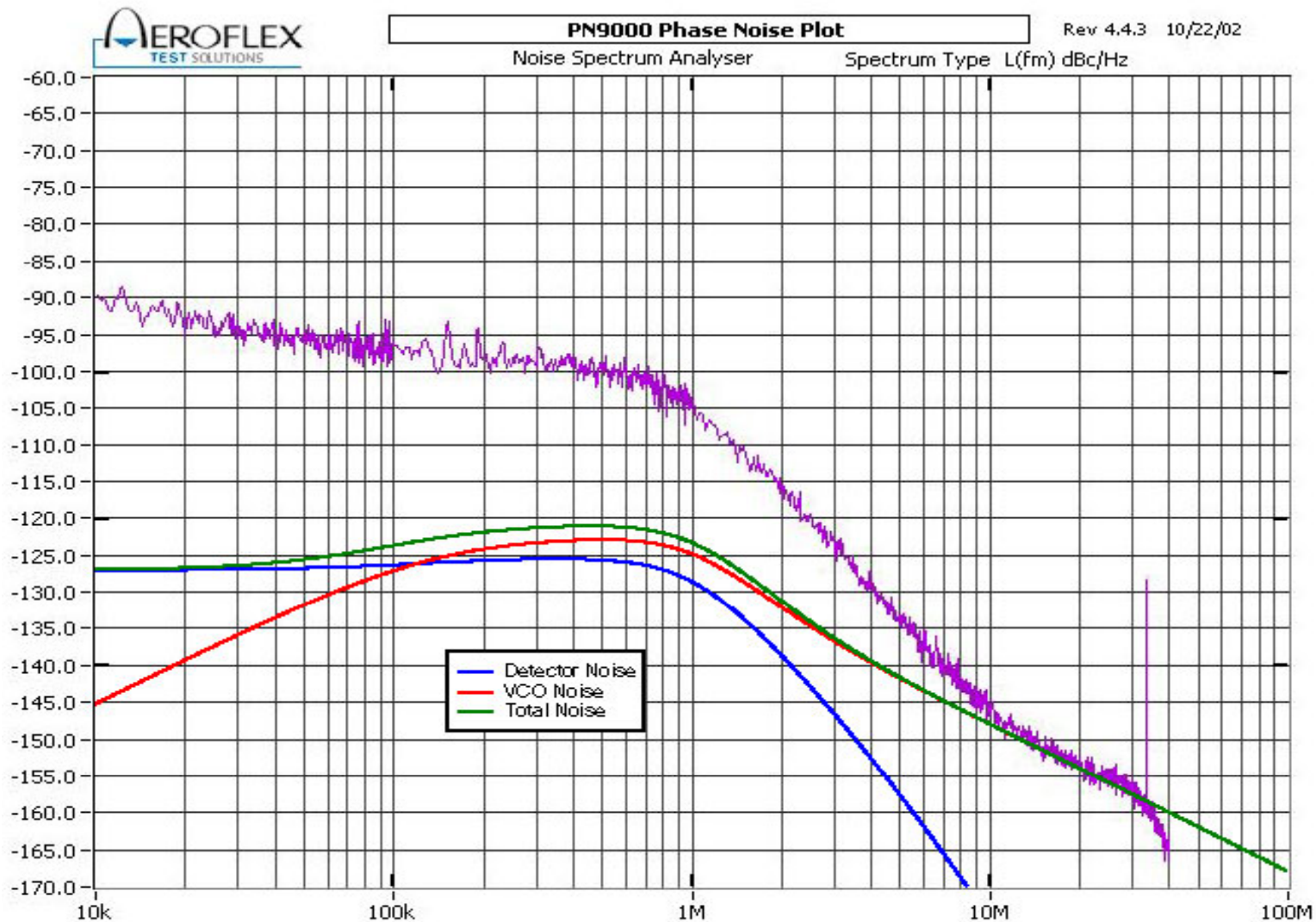
# Measured Phase Noise of Intrinsic Noise Sources




- IC configured as integer-N synth for above measurement
  - The detector noise calculation is way off!
 
# Adjustment of Calculations to Fit Measured Result




- Calculated noise above assumes:
  - Detector noise is -103 dBc/Hz at low freq
 
# Measured Phase Noise of 2<sup>nd</sup> order $\Sigma$ - $\Delta$ Synthesizer




- Calculations match measured results reasonably well
  - Note: Sampler is active for this measurement
 
# Measured Phase Noise of 7-bit PFD/DAC Synthesizer




- Calculations match measured results reasonably well
 
# Comparison of Measured 2<sup>nd</sup> Order $\Sigma$ - $\Delta$ to PFD/DAC




**Suppression Plot**

 

- Measured 7-bit PFD/DAC quantization noise suppression is *better* than 25 dB!
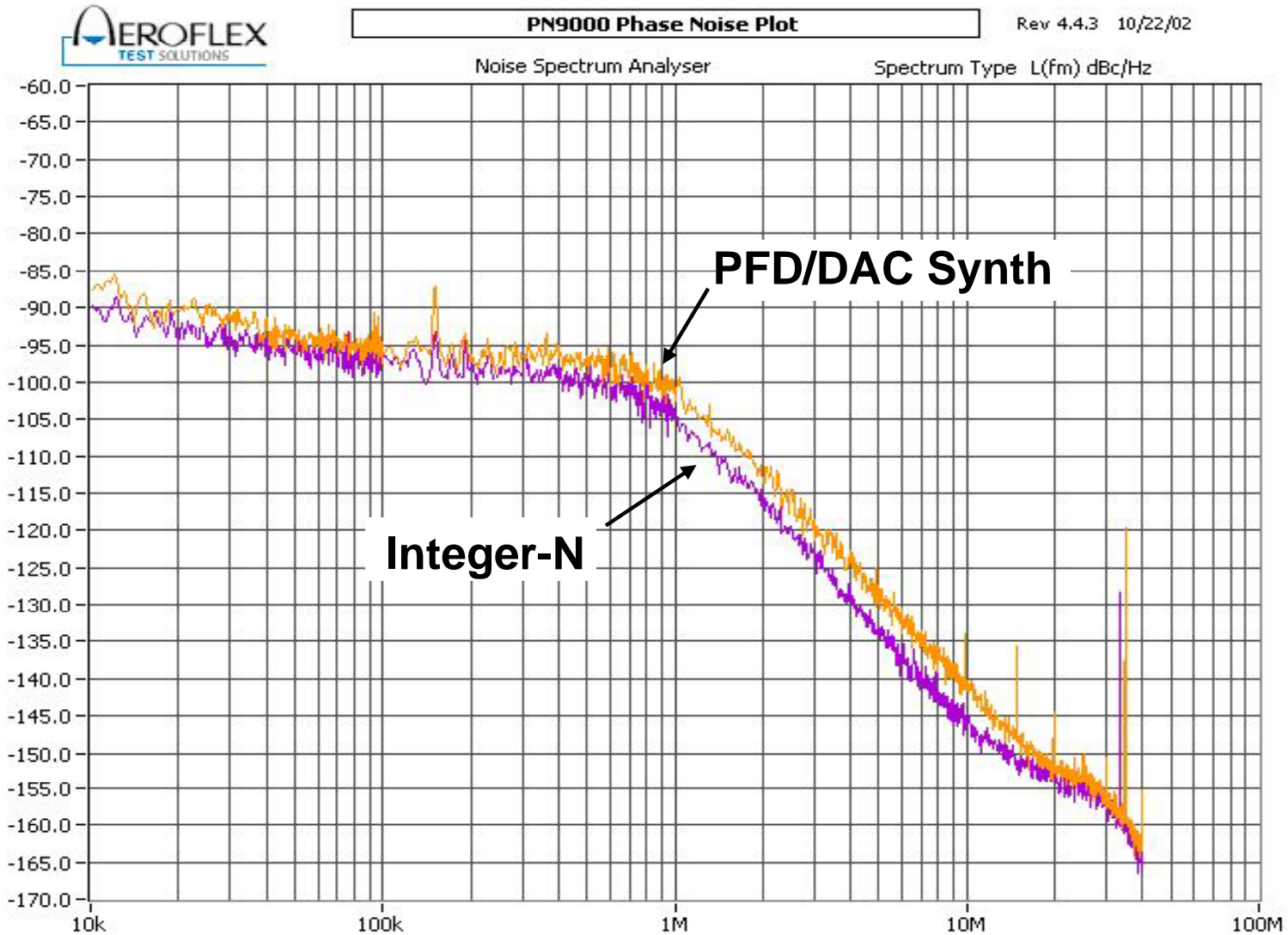
# Comparison of Measured Integer-N to PFD/DAC




- **7-bit PFD/DAC approach is within 5 dB of intrinsic noise performance of PLL**

# ***Summary of Calculation/Measured Results Comparison***

---

- **Comparison of PLL Design Assistant results to measured data allow back extraction of key parameters:**
  - **Intrinsic noise**
    - Detector and VCO noise
  - **PFD/DAC nonidealities**
    - Delay mismatch value
- **Future work: better low frequency noise accuracy**

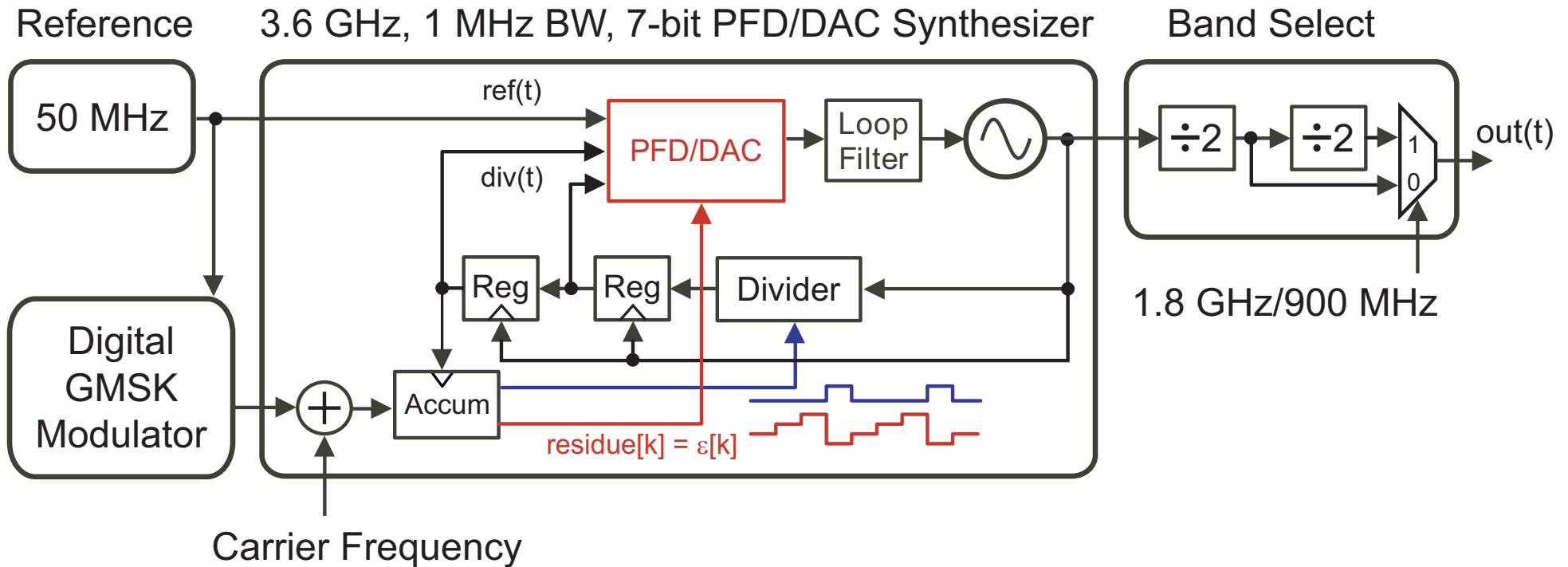
# A Highly Digital Implementation of a GMSK Transmitter




- **A fractional-N frequency synthesizer provides highly accurate phase/frequency modulation capability**
  - Multiple carrier frequencies easily achieved with digital frequency division
  - N-bit PFD/DAC extends achievable data rate for a given noise performance (at higher frequency offsets)
 
# GMSK Eye Diagrams at 271 kbit/s (~900 MHz Carrier)

Sim Simulated Eye Diagrams for Cell: wb\_synth\_overall\_system, Lib: WBSynth\_Example, Sim: t



- Measured
- HP 89441 Vec. Analyzer

 


- CppSim simulation
- 100e6 points: < 44 min

**Close agreement between simulated and measured results!**

 
# GMSK Spectra Plots at 271 kbit/s (~900 MHz Carrier)

Simulated Modulated PLL Spectrum for Cell: wb\_synth\_overall\_system, Lib: WBSynth\_Example, :





- **CppSim simulation**
  - 100e6 points: < 44 min

 - **Measured**
  - **HP 8563E**  
**Spectrum Analyzer**



  
# GMSK Eye Diagrams at 500 kbit/s (~900 MHz Carrier)

Sim Simulated Eye Diagrams for Cell: wb\_synth\_overall\_system, Lib: WBSynth\_Example, Sim: t




- **CppSim simulation**
  - 100e6 points: < 44 min

 - **Measured**
  - HP 89441 Vec. Analyzer



 
# GMSK Spectra Plots at 500 kbit/s (~900 MHz Carrier)

Simulated Modulated PLL Spectrum for Cell: wb\_synth\_overall\_system, Lib: WBSynth\_Example, :





- **CppSim simulation**
  - 100e6 points: < 44 min

 - **Measured**
  - **HP 8563E**  
**Spectrum Analyzer**



  
# GMSK Eye Diagrams at 1 Mbit/s (~900 MHz Carrier)

Sim Simulated Eye Diagrams for Cell: wb\_synth\_overall\_system, Lib: WBSynth\_Example, Sim: t




- CppSim simulation
  - 100e6 points: < 44 min

- Measured
  - HP 89441 Vec. Analyzer

 

 
# GMSK Spectra Plots at 1 Mbit/s (~900 MHz Carrier)

Simulated Modulated PLL Spectrum for Cell: wb\_synth\_overall\_system, Lib: WBSynth\_Example, :









- **CppSim simulation**
  - 100e6 points: < 44 min

 - **Measured**
  - **HP 8563E**  
**Spectrum Analyzer**


      
# GMSK Measured Data at ~1.8 GHz Carrier Frequency



**271 kbit/s**

**500 kbit/s**

**1 Mbit/s**

# Conclusions

---

- **Fractional-N frequency synthesizers are about to undergo dramatic improvement in achieving high PLL bandwidth with excellent noise performance**
  - **The PFD/DAC approach presented here is only one of many possibilities to achieve this goal**
- **Design and simulation methodologies are starting to emerge**
  - **Analytical modeling of noise can be quite accurate**
    - **The PLL Design Assistant can be useful in this area**
  - **Behavioral simulation can be used to verify analytical models**
    - **CppSim offers a convenient and fast framework for this**

**Research into High Bandwidth PLL Architectures is at an Exciting Crossroads**