

Design Techniques for Analog PLLs: Moving Beyond Classical Topologies

CICC 2010


Michael Perrott

September 2010

Copyright © 2010 by Michael H. Perrott


All rights reserved.

What is a Phase-Locked Loop (PLL)?

 

- VCO efficiently provides oscillating waveform with variable frequency
- PLL synchronizes VCO frequency to input reference frequency through feedback
 - Key block is phase detector
 - Realized as *digital gates* that create pulsed signals


Integer-N Frequency Synthesizers

 

- Use digital counter structure to divide VCO frequency
 - Constraint: must divide by integer values
- Use PLL to synchronize reference and divider output

Output frequency is digitally controlled


Fractional-N Frequency Synthesizers

 


- Dither divide value to achieve fractional divide values
 - PLL loop filter smooths the resulting variations

Very high frequency resolution is achieved


The Issue of Quantization Noise

 

 - Limits PLL bandwidth
- Increases linearity requirements of phase detector




Analog Phase Detection

 



- Phase detector varies pulse width with phase error
- Loop filter smooths pulses to extract average value

Issues with Analog Loop Filter

 

- Charge pump: output resistance, mismatch, noise, leakage
 - Analog design requires significant effort, hard to port
- RC Network: large area

Should We Go All Digital ?

  

Staszewski et. al.,
TCAS II, Nov 2003


- **Digital loop filter: compact area, digital flow**
- **Issue: difficult to achieve low area and power in older processes such as 0.18u CMOS**
 - May not be worth the effort unless advanced CMOS available

Can We Achieve an Analog PLL with Lower Design Complexity and Adequate Performance?

Outline

- **Background information on traditional analog PLL implementations and analysis**
- **Moving away from the traditional approach**
 - XOR-based phase detection
 - Switched resistor loop filter
 - Switched capacitor frequency detection
- **MEMS oscillator example**



Key Characteristics of a Phase Detector

 

- Adequate phase detection range
 - Fractional-N PLLs need more range than Integer-N PLLs
- Linearity across operating range of phase detector
 - Fractional-N PLLs have issues with noise folding


XOR Phase Detector

  - Creates pulse widths that vary according to the phase difference between reference and divider output signals
- Simple implementation
- Divide-by-2 is used to eliminate impact of falling edges
 - Duty cycle of Ref(t) and Div(t) signals is no longer of concern



Modeling of XOR Phase Detector

 - Average value of pulses is extracted by loop filter
 - Look at detector output over one cycle:




- Equation:

$$\text{avg}\{e(t)\} = -1 + 2\frac{W}{T}$$

Notice that the average error is a *linear* function of the pulse width W regardless of mismatch

 
Overall XOR Phase Detector Characteristic




Gain flips in sign according to phase error region of phase detector

Modeling of XOR Phase Detector

 
- Assume phase difference is confined to same slope region
 - XOR PD model becomes a highly linear gain element



- Corresponding frequency-domain model

 

 Overall PLL Model with XOR Phase Detector




- Define $A(f)$ as *open loop response*

$$A(f) = K_{pd}H(f) \left(\frac{K_v}{jf} \right) \frac{1}{N}$$


- Where K_{pd} is defined as PD gain ($1/\pi$ for XOR PD)
- Define $G(f)$ as a parameterizing *closed loop function*

$$G(f) = \frac{A(f)}{1 + A(f)}$$

Key Properties of $G(f)$ Function

 

 
$$A(f) = K_{pd}H(f) \left(\frac{K_v}{jf} \right) \frac{1}{N}$$



$$G(f) = \frac{A(f)}{1 + A(f)}$$

- **$G(f)$ always has a DC gain of 1**
 - True since $A(f)$ goes to infinity as f goes to 0
- **$G(f)$ is lowpass in nature**
 - True since $A(f)$ goes to 0 as f goes to infinity
- **$G(f)$ has bandwidth close to unity gain frequency of $A(f)$**

 
Closed Loop Response From Ref to PLL Output



$$\begin{aligned} \frac{\Phi_{out}}{\Phi_{ref}} &= \frac{K_{pd}H(f)K_v/(jf)}{1 + (1/N)K_{pd}H(f)K_v/(jf)} \\ &= N \frac{(1/N)K_{pd}H(f)K_v/(jf)}{1 + (1/N)K_{pd}H(f)K_v/(jf)} \\ &= N \frac{A(f)}{1 + A(f)} = \boxed{NG(f)} \end{aligned}$$

Lowpass with DC gain of N

 
Closed Loop Response From PD to PLL Output



$$\begin{aligned} \frac{\Phi_{out}}{e_n} &= \frac{H(f)K_v/(jf)}{1 + (K_{pd}/N)H(f)K_v/(jf)} \\ &= \frac{N}{K_{pd}} \frac{(K_{pd}/N)H(f)K_v/(jf)}{1 + (K_{pd}/N)H(f)K_v/(jf)} \\ &= \frac{N}{K_{pd}} \frac{A(f)}{1 + A(f)} = \boxed{\frac{N}{K_{pd}} G(f)} \end{aligned}$$

Lowpass with DC gain of N/K_{pd}

 Closed Loop Response From VCO to PLL Output




$$\frac{\Phi_{out}}{\Phi_{vn}} = \frac{1}{1 + (K_{pd}/N)H(f)K_v/(jf)}$$


$$= \frac{1}{1 + A(f)} = 1 - \frac{A(f)}{1 + A(f)} = \boxed{1 - G(f)}$$

Highpass with high frequency gain of 1

Consider A First Order Loop Filter

 


■ First order loop filter

 


$$\Rightarrow H(f) = \frac{1}{1 + jf/f_p}$$

Closed Loop Poles Versus Open Loop Gain

Evaluation of Phase Margin

 


Closed Loop Pole Locations of $G(f)$

 

- Higher open loop gain leads to an increase in bandwidth but decrease in phase margin
 - Closed loop poles start exhibiting higher Q


Corresponding Closed Loop Response

 

- **Decrease in phase margin leads to**
 - **Peaking in closed loop frequency response**
 - **Ringling in closed loop step response**

Design of PLL dynamics is similar to opamps and other classical feedback systems

 The Problem with a First Order Loop Filter



$$A(f) = K_{pd}H(f) \left(\frac{K_v}{jf} \right) \frac{1}{N}$$



$$G(f) = \frac{A(f)}{1 + A(f)}$$


- Recall that bandwidth of $G(f)$ is roughly the same as unity gain frequency of $A(f)$

- To achieve good phase margin, $f_p \gg$ unity gain frequency
 - Implies that $H(f) \approx 1$ at unity gain frequency
 - Bandwidth of $G(f)$ purely set by K_{pd} , K_v , and N

Limited freedom to choose desired closed loop bandwidth

Inclusion of a Charge Pump

 - Charge pump current adds a new parameter that allows more freedom in choosing the PLL bandwidth
- Lead/lag filter is a common loop filter with charge pump
 - Current into a capacitor forms integrator
 - Add extra pole/zero using resistor and additional capacitor



Forms a Type II PLL

$$H(f) = \left(\frac{I_{cp}}{sC_{sum}} \right) \frac{1 + jf/f_z}{1 + jf/f_p}$$


■ **Where:**

$$C_{sum} = C_1 + C_2$$

$$f_z = \frac{1}{2\pi R_1 C_2}$$

$$f_p = \frac{C_1 + C_2}{2\pi R_1 C_1 C_2}$$

 
Type I versus Type II PLL Implementations




- **Type I: one integrator in PLL open loop transfer function $A(f)$**
 - VCO adds one integrator
 - Loop filter, $H(f)$, has no integrators
- **Type II: two integrators in PLL open loop transfer function $A(f)$**
 - Loop filter, $H(f)$, has one integrator

VCO Input Range Issue for Type I PLL Implementations

 - DC output range of gain block versus integrator



 - Issue: often need to provide attenuation through loop filter to achieve a desired closed loop bandwidth
 - Loop filter output fails to cover full input range of VCO




Options for Achieving Full Range Span of VCO

■ Type I


- Add a D/A converter to provide coarse tuning
 - Adds power and complexity
 - Steady-state phase error inconsistently set

■ Type II

 - Integrator automatically provides DC level shifting
 - Low power and simple implementation
 - Steady-state phase error always set to zero





Design of Type II, Charge Pump PLL

 

- Place f_z and f_p based on phase margin, and open loop gain based on desired PLL bandwidth
 - Charge pump offers high flexibility in choosing PLL bandwidth

  
Negative Issues For Type II PLL Implementations



- **Parasitic pole/zero pair causes**
 - **Peaking in the closed loop frequency response**
 - Increases PLL phase noise
 - **Extended settling time due to parasitic “tail” response**
 - Bad for applications demanding fast settling time

The Need for Frequency Detection


Response of PLL to Divide Value Changes

 

- Change output frequency by changing the divide value
- Classical approach provides no direct model of impact of divide value variations
 - Treat divide value variation as a perturbation to a linear system and use the PLL closed loop response
- More advanced PLL models include divide value variations
 - M.H. Perrott, M.D. Trott, C.G. Sodini, "A modeling approach for Σ - Δ fractional-N frequency synthesizers allowing straightforward noise analysis," JSSC, vol. 37, pp. 1028-1038, Aug. 2002.

Response of an Actual PLL to Divide Value Change

 
- **Example: Change divide value by one**



- **PLL responds according to linear model of closed loop response!**


What Happens with Large Divide Value Variations?

- PLL response does not fit linear model

 

- What is happening here?


Recall Phase Detector Characteristic

 


- To simplify modeling, we assumed that we always operated in a confined phase range (0 to 2π)
 - Led to a simple PD model
- Large perturbations knock us out of that confined phase range
 - PD behavior varies depending on the phase range it happens to be in

Cycle Slipping

 - Consider the case where there is a frequency offset between divider output and reference
 - We know that phase difference will accumulate




 - Resulting ramp in phase causes PD characteristic to be swept across its different regions (cycle slipping)




Impact of Cycle Slipping

 - Loop filter averages out phase detector output
- Severe cycle slipping causes phase detector to alternate between regions very quickly
 - Average value of XOR characteristic can be close to zero
 - PLL frequency oscillates according to cycle slipping
 - In severe cases, PLL will not re-lock
 - PLL has finite frequency lock-in range!



Back to PLL Response Shown Previously


 
- PLL output frequency indeed oscillates
 - Eventually locks when frequency difference is small enough



- How do we extend the frequency lock-in range?


Phase Frequency Detectors (PFD)

■ Example: Tristate PFD

  

Tristate PFD Characteristic

 
- Calculate using similar approach as used for XOR phase detector




- Note that phase error characteristic is asymmetric about zero phase
 - Key attribute for enabling frequency detection

PFD Enables PLL to Always Regain Frequency Lock

 - **Asymmetric phase error characteristic allows positive frequency differences to be distinguished from negative frequency differences**
 - Average value is now positive or negative according to sign of frequency offset
 - PLL will always relock for type II PLL




The Issue of Noise

 


- Each PLL component contributes noise that impacts overall PLL output phase noise
- Achievement of adequately low PLL phase noise is a key issue when designing a PLL

 Modeling the Impact of Noise on Output Phase of PLL




- **Determine impact on output phase by deriving transfer function from each noise source to PLL output phase**
 - There are a lot of transfer functions to keep track of!

Simplified Noise Model

 

- Refer all non-VCO PLL noise sources to the PFD output
 - PFD-referred noise corresponds to the sum of these noise sources referred to the PFD output
 - Typically, charge pump noise dominates PFD-referred noise

 Leverage Previous Transfer Function Analysis



■ PFD-referred noise

- Lowpass with DC gain of N/K_{pd}


$$\frac{\Phi_{out}}{e_n} = \frac{N}{K_{pd}} G(f)$$

■ VCO-referred noise

- Highpass with gain of 1



$$\frac{\Phi_{out}}{\Phi_{vn}} = 1 - G(f)$$

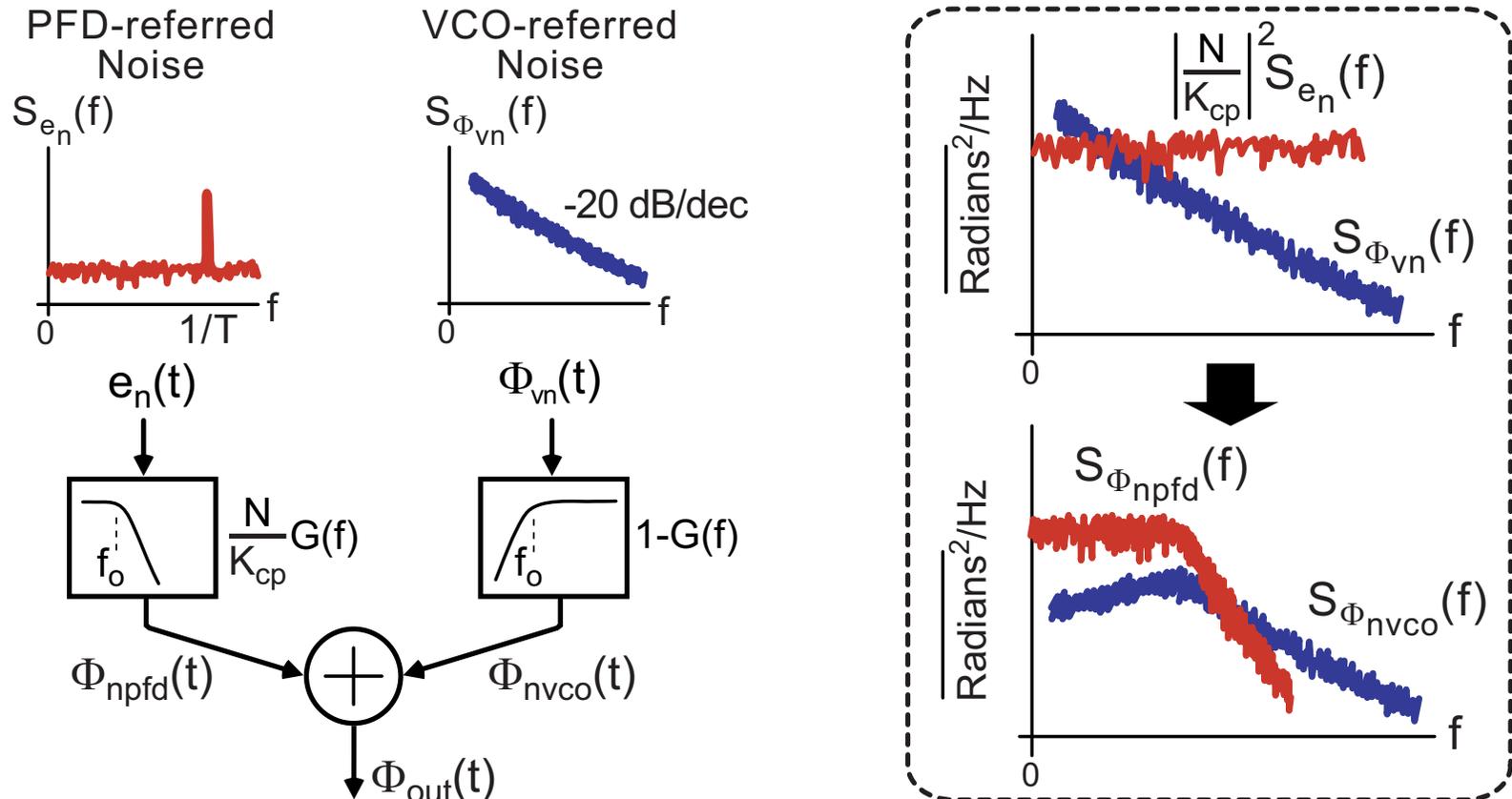Transfer Function View of PLL Phase Noise



- **PFD-referred noise dominates at low frequencies**
 - Corresponds to close-in phase noise of synthesizer
- **VCO-referred noise dominates at high frequencies**
 - Corresponds to far-away phase noise of synthesizer

  Spectral Density of PLL Phase Noise Components



■ PFD-referred noise:

$$S_{\Phi_{npfd}}(f) = \left| \frac{N}{K_{pd}} G(f) \right|^2 S_{\Phi_{en}}(f)$$


■ VCO-referred noise:

$$S_{\Phi_{nvco}}(f) = |1 - G(f)|^2 S_{\Phi_{vn}}(f)$$

■ Overall:

$$S_{\Phi_{out}}(f) = S_{\Phi_{npfd}}(f) + S_{\Phi_{nvco}}(f)$$


Take a Closer Look at Charge Pump Noise

 

- Spectral density of charge pump noise is a function of device noise and pulse width
 - Short pulse widths reduce effective charge pump noise

Tristate PFD has an advantage of allowing short pulse widths (i.e., lower noise) during steady-state operation

 Impact of Transistor Current Magnitude on Noise



- Charge pump noise will be related to the current it creates as


$$S_{I_{cpn}}(f) \propto \frac{\overline{I_{cp}^2}}{\Delta f} = 4kT\gamma g_{do}$$

- Recall that g_{do} is the channel resistance at zero V_{ds}
 - At a fixed current density, we have

$$g_{do} \propto \sqrt{I_{cp}W} \propto I_{cp} \Rightarrow S_{I_{cpn}}(f) \propto I_{cp}$$

- Therefore, charge pump noise is proportional to I_{cp}


Analysis of Charge Pump Noise Impact

 

- Transfer function from charge pump noise to PLL output is found by referring noise to PFD output by factor $1/I_{cp}$

$$\frac{\Phi_{out}}{I_{cpn}} = \left(\frac{1}{I_{cp}} \right) \frac{\Phi_{out}}{e_n} = \left(\frac{1}{I_{cp}} \right) \frac{N}{K_{pd}} G(f)$$

 
Increasing I_{cp} Leads to Reduced Noise at PLL Output



- Output phase noise due to charge pump:

$$S_{\Phi_{out}}(f) = \left| \left(\frac{1}{I_{cp}} \right) \frac{N}{K_{pd}} G(f) \right|^2 S_{I_{cpn}}(f) \propto \left| \frac{1}{I_{cp}} \right|^2 I_{cp} \propto \frac{1}{I_{cp}}$$

 
Issue: Increasing I_{cp} Leads to Larger Loop Filter



- To keep PLL BW unchanged, assume $I_{cp}/(C_1 + C_2)$ is held constant (to maintain open loop gain)

Area gets larger since increasing I_{cp} leads to increased loop filter capacitance $(C_1 + C_2)$

 
Better Approach: Increase PD Gain to Lower Noise



- To keep PLL BW unchanged, assume $I_{cp}K_{pd}$ held constant
 - Loop filter can remain *unchanged* as K_{pd} is increased




$$S_{\Phi_{out}}(f) = \left| \left(\frac{1}{I_{cp}} \right) \frac{N}{K_{pd}} G(f) \right|^2 S_{I_{cpn}}(f) \propto I_{cp} \propto \frac{1}{K_{pd}}$$

 Can We Increase PD Gain for a Charge Pump PLL?




- **XOR-based PD provides factor of two higher gain than a tristate PFD**
 - Key issue: carries an overall noise penalty since the charge pump is never gated off (i.e., generates long pulses)
 - XOR PD rarely used due to its noise penalty

   Key Issue of Tristate PFD: Charge Pump Mismatch




- Mismatch of charge pump Up/Down currents leads to nonlinearity in the PLL phase comparison path when tristate PFD used

 Nonlinearity Causes Noise Folding with Frac-N PLLs



■ Significant analog design effort is often required to avoid this issue




Summary of Charge Pump PLL Issues

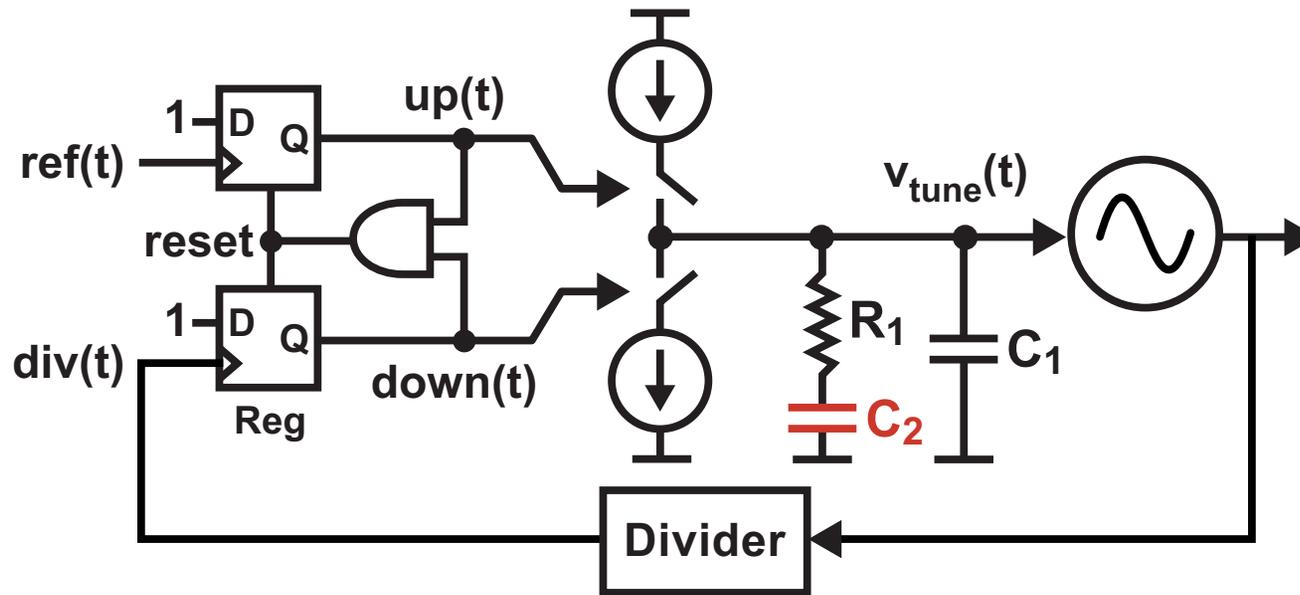

- **Tristate PFD has issues with**
 - Low PD gain – leads to increased loop filter for given PLL noise
 - Charge pump nonlinearity – causes quantization noise folding
- **Charge Pump has issues with**
 - Nontrivial analog design effort for wide range, high output impedance, low leakage, reasonable matching, low noise


Are there alternative analog PLL architectures?

How Do We Achieve Higher PD Gain?

   

- Use tristate PD as our starting point
 - Range of detector spans 2 Reference periods (i.e., 4π radians)
 - PD gain is $2/(\text{PD range}) = 2/(4\pi) = 1/(2\pi)$

Sampled PD Achieves Much Higher PD Gain

 


Gao, Klumperink, Bohsali, Nauta, JSSC, Dec 2009

- **Directly sample VCO signal at reference edges**
 - PD gain becomes $2/(\pi/N) = 2N/\pi$ assuming
 - $N = \text{VCO Frequency} / (\text{Ref Frequency})$
 - PD output voltage range assumed to be -1 to 1



Yields much lower in-band PLL noise, but constrained to integer-N PLL structures

 Achieving Higher PD Gain for a Fractional-N PLL




- Develop a PD with reduced phase error range in which Up/Down pulses vary in width in opposite directions
 - Need an appropriate loop filter topology that properly leverages the reduced PD range for higher PD gain

  Key Implementation Detail: Use Switched Resistor




 
See also:
 Hedayati, Bakkaloglu
 RFIC 2009




- Switching to voltage Supply/Gnd causes $V_{c1}(t)$ to reflect the average of the Up/Down pulses *within* the reduced PD range
 - PD gain is increased since full voltage range at V_{c1} achieved across a reduced phase error range

Implementation of High Gain Phase Detector

  Delay Buffer For Non-Overlapping Up/Down Pulses





Phase Detector Characteristic

 


- Use 4X higher divider frequency
 - Simple digital implementation

  
Multi-Phase Pulse Generation (We'll Use it Later...)



Phase Detector Characteristic

 


 What If We Use A Charge Pump with the High Gain PD?




- **PD Gain increased by 2 compared to tristate PFD**
 - Reduced phase error range and max/min current occurs
- **High linearity despite charge pump current mismatch**
 - Similar to XOR PD, but noise is reduced

 Increasing Feedforward Gain While Utilizing Charge Pump




See also:
Craninckx,
JSSC, Dec
1998

 - We can use the high gain PD in a dual-path loop filter topology
 - But we want a simple design!




Can we remove the charge pump to reduce the analog design effort?

 
Passive RC Network Offers a Simpler Implementation




 
- Capacitive feedforward path provides stabilizing zero
- Design effort is simply choosing switch sizes and RC values



The Issue of Reference Spurs

 

Leverage Multi-Phase Pulsing

  


Ripple from Up/Down pulses blocked before reaching VCO

- Reference spurs reduced!
- Similar to sample-and-hold technique (such as Zhang et. al., JSSC, 2003)

There is a nice side benefit to pulsing resistors...

Pulsing Resistor Multiplies Resistance!

 


J. A. Kaehler, JSSC, Aug. 1969
and
P. Kurahashi, P. K. Hanumolu,
G. C. Temes, and U.-K. Moon,
JSSC, Aug. 2007

$$R_{\text{eff}} = \frac{T_{\text{period}}}{T_{\text{on}}} R$$

- Resistor only passes current when pulsed on
 - Average current through resistance is reduced according to ratio of On time, T_{on} , versus pulsing Period, T_{period}
 - *Effective* resistance is actual resistance *multiplied* by ratio $T_{\text{period}}/T_{\text{on}}$

Resistor multiplication allows a large RC time constant to be implemented with smaller area

 
Parasitic Capacitance Reduces Effective Resistance



- Parasitic capacitance stores charge during the pulse “On” time
 - Leads to non-zero current through resistor during pulse Off time
 - Effective resistance reduced



Spice simulation and measured results reveal that >10X resistor multiplication can easily be achieved

 Multi-Modulus Divider Allows Short Pulse Generation




- **Creates well controlled pulse widths corresponding to multiples of the period of its high speed input**
 - Standard circuit used in many fractional-N PLL structures
 - Pulse width can be changed by tapping off different stages

  Utilize Short Pulses from Divider in the High Gain PD




- Short pulses from divider output are used to clock the PD registers
- PD state is used to gate divider output every 4 cycles to form Last pulse
 - Lower pulse frequencies can also be implemented

 Switched Resistor Achieves PLL Zero with Low Area




 - For robust stability, PLL zero should be set \ll PLL BW
 - Example: PLL BW = 30kHz
 - Assume desired $w_z = 4$ kHz
 - Set $C_f = 2.5$ pF (for low area)
 - Required $R_{3_eff} = 16$ MegaOhms
 - Large area




Example: Proper choice of T_{on} and T_{period} allows $R_{3_eff} = 16$ MegaOhms to be achieved with $R_3 = 500$ kOhms!

Overall Design of Loop Filter

 



- Apply standard transfer function analysis to achieve desired PLL bandwidth and phase margin

 Noise Analysis (Ignore Parasitic Capacitance of Resistors)




- **Assumption: switched resistor time constants are much longer than “on time” of switches**
 - Single-sided voltage noise contributed by each resistor is simply modeled as $4kTR_{eff}$ (same as for a resistor of the equivalent value)
- **Note: if switched resistor time constants are shorter than “on time” of switches**
 - Resistors contribute kT/C noise instead of $4kTR_{eff}$
 - We would not want to operate switched resistor filter in this domain since time constants would not be boosted

  Issue: Nonlinearity in Switched Resistor Loop Filter



- **Nonlinearity is caused by**
 - Exponential response of RC filter to pulse width modulation
 - Variation of T_{hold} due to Sigma-Delta dithering of divide value
- **Note: to avoid additional nonlinearity, design divide value control logic to keep T_{on} a constant value**

 Nonlinearity Due to Pulse Width Modulation



Pulse width modulation nonlinearity is reduced as ratio $\Delta T/(R_1 C_1)$ is reduced


- If $\Delta T/(R_1 C_1)$ is small:

$$e^{\frac{1}{R_1 C_1} \Delta T} \approx 1 + \frac{\Delta T}{R_1 C_1}$$

- This implies nonlinearity is reduced with lower PLL bandwidth


$$V_{c1}[k] = -V_{dd} e^{-\frac{1}{R_1 C_1} \frac{T_{div}}{2}} e^{\frac{1}{R_1 C_1} \Delta T} + e^{-\frac{T_{div}}{R_1 C_1}} V_{c1}[k-1] + V_{dd}$$

 Key Design Issue: Folded Noise versus Other Noise




- **Folded quantization noise due to nonlinearity is reasonably below other noise sources for this example**
 - However, could be an issue for wide bandwidth PLLs
- **Use (CppSim) behavioral simulation to evaluate this issue**

 The Issue of Initial Frequency Acquisition




- During initial frequency acquisition, $V_{tune}(t)$ must be charged to proper bias point
 - Following through on previous example:
 - Large 16 MegaOhm resistance of R_{3_eff} prevents fast settling of the voltage across C_3

 Capacitive Divider Sets Instantaneous Voltage Range




How do we quickly charge capacitor C_3 to its correct DC operating point during initial frequency acquisition?

 Utilize Switched Capacitor Charging Technique



- Charge C_3 high or low only when frequency error is detected
 - No steady-state noise penalty, minimal power consumption

 
CppSim Behavioral Simulation of Frequency Locking




Switched capacitor technique allows relatively fast frequency locking

PLL Application: A MEMS-based Programmable Oscillator

Quartz Oscillators

 

MEMS-based Oscillator

 


- A part for each frequency and non-plastic packaging
 - Non-typical frequencies require long lead times

- Same part for all frequencies and plastic packaging
 - Pick any frequency you want without extra lead time


We can achieve high volumes at low cost using IC fabrication

 Architecture of MEMS-Based Programmable Oscillator




- **MEMS device provides high Q resonance at 5 MHz**
 - CMOS circuits provide DC bias and sustaining amplifier
- **Fractional-N synthesizer multiplies 5 MHz MEMS reference to a programmable range of 750 to 900 MHz**
- **Programmable frequency divider enables 1 to 115 MHz output**

Compensation of Temperature Variation

 

- High resolution control of fractional-N synthesizer allows simple method of compensating for MEMS frequency variation with temperature
 - Simply add temperature sensor and digital compensation logic

 
Why Use An Alternative Fractional-N PLL Structure?



Want to achieve low area, low power, and low design complexity


Switched resistor PLL provides a nice solution for this application space

 CMOS and MEMS Die Photos Show Low Area of PLL




- Active area:
 - VCO & buffer & bias: 0.25mm²
 - PLL (PFD, Loop Filter, divider): 0.09 mm²
 - Output divider: 0.02 mm²
- External supply
 - 1.8/3.3V
- Current (20 MHz output, no load)
 - ALL: 3.2/3.7mA
 - VCO: 1.3mA
 - PLL & Output Divider: 0.7mA

Measured Phase Noise (100 MHz output)

 


- Suitable for most serial applications, embedded systems and FPGAs, audio, USB 1.1 and 2.0, cameras, TVs, etc.

 Calculated Phase Noise Profile of Overall PLL




- Note that loop filter noise is well below other PLL noise sources

 Simulated Impact of Switched Resistor Nonlinearity



- **Noise folding below other PLL noise sources**
 - More significant for third order Sigma-Delta

 Frequency Variation After Single-Temperature Calibration



**< +/-30 ppm across industrial temperature range
with single-temperature calibration**

Conclusion

- **We took a closer look at the classical charge pump PLL**
 - Very versatile structure
 - Requires a fair amount of analog design effort
- **Alternative PLL structures can provide low area, low power, and reduced analog design effort**
 - High gain phase detector lowers impact of loop filter noise
 - Switched resistor technique eliminates the charge pump and reduces area through resistor multiplication
 - Switched capacitor frequency detection enables reasonable frequency acquisition time with no noise penalty

Application specific PLL structures can provide worthwhile benefits over a classical analog PLL structure